
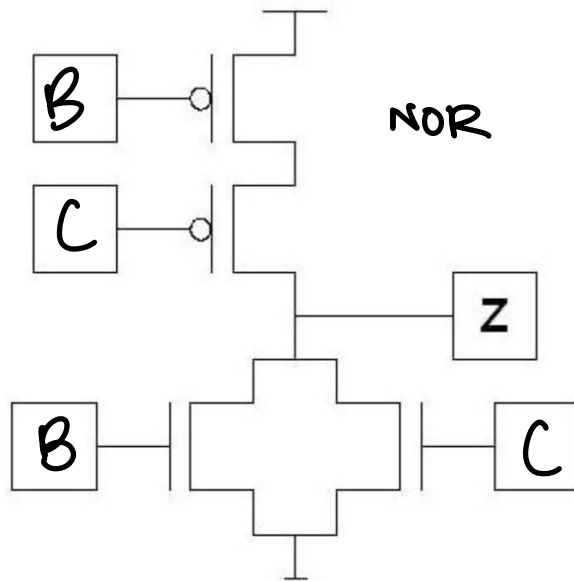
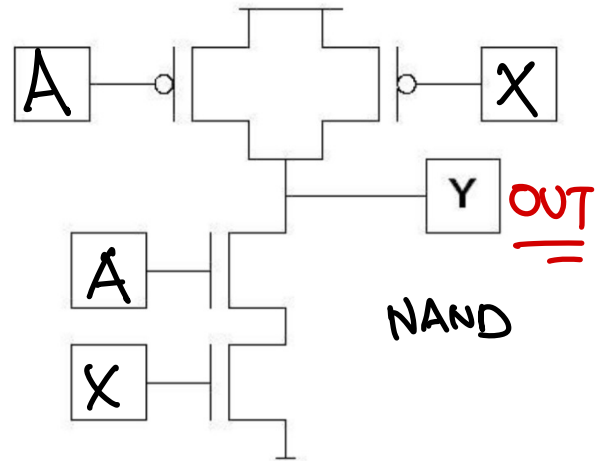


①

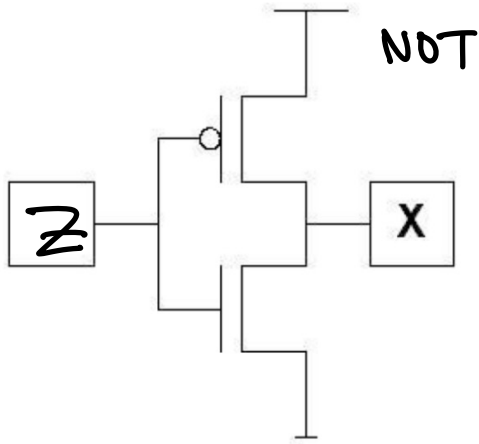

$$\begin{aligned} & \text{NOT}(A \text{ AND } (B \text{ OR } C)) \\ & A \text{ NAND } (B \text{ OR } C) \\ & A \text{ NAND NOT}(B \text{ NOR } C) \end{aligned}$$

②

$$(A'B'C')' = A + B + C$$

3-input OR gate

DeMorgan's Law

③

$$2^5 = 32$$

$$2^n$$

$$\lceil \log_2 9 \rceil$$

$$\lceil \log_2 n \rceil$$

④

A	B	C	D	out
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

outputs of 1 have inputs that
sum to 1 or 3.


outputs of 0 have inputs that
sum to 2.

5


	A	B	C	Y	Z
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	1
3	0	1	1	0	1
4	1	0	0	1	1
5	1	0	1	0	1
6	1	1	0	0	0
7	1	1	1	1	0

$$Y = \bar{A}\bar{B}'C + \bar{A}BC' + A\bar{B}'C' + ABC$$
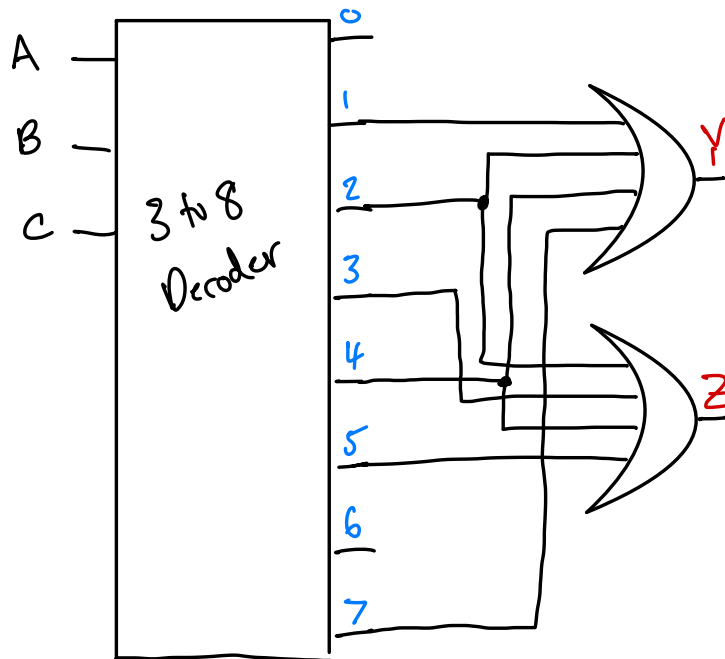
$$Z = \bar{A}BC' + \bar{A}BC + A\bar{B}'C' + A\bar{B}'C$$



6

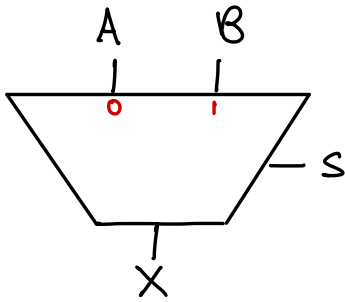


A	B	S	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$$X = A'BS + AB'S' + ABS' + ABS$$

$$BS(A' + A) + AS'(B' + B)$$


$$BS + AS'$$

7

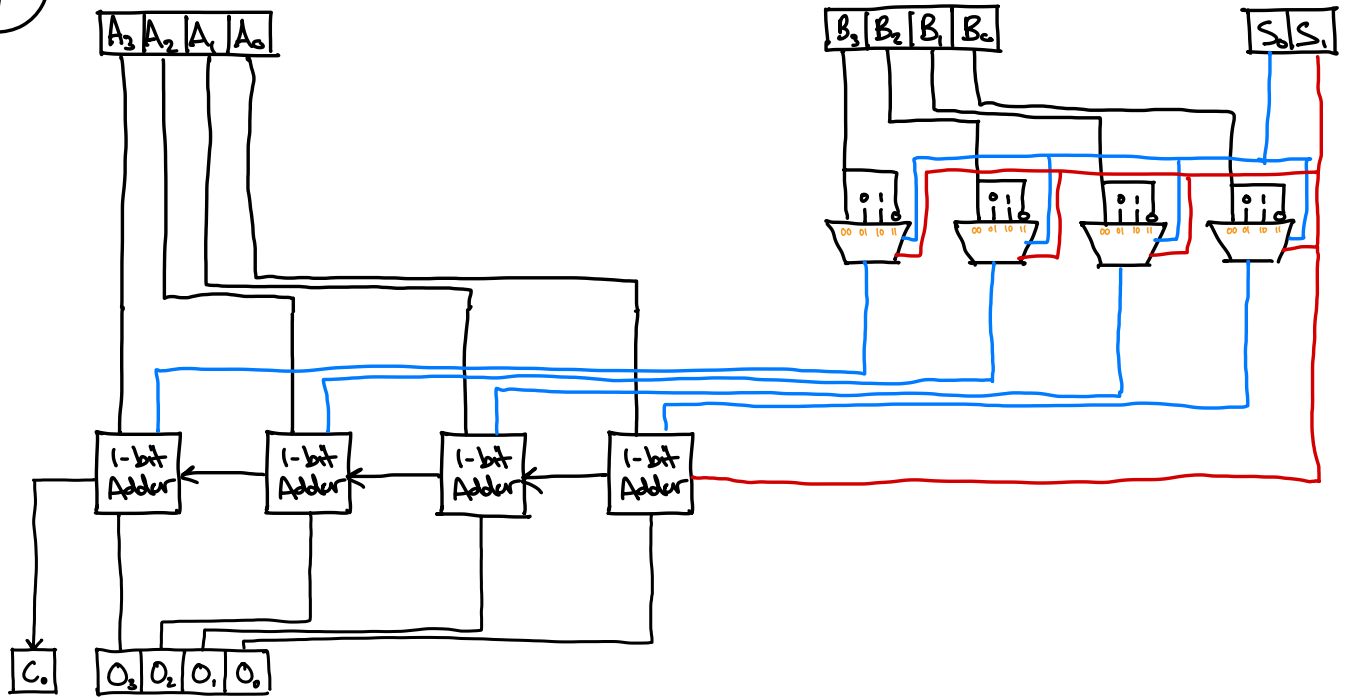


8

a)

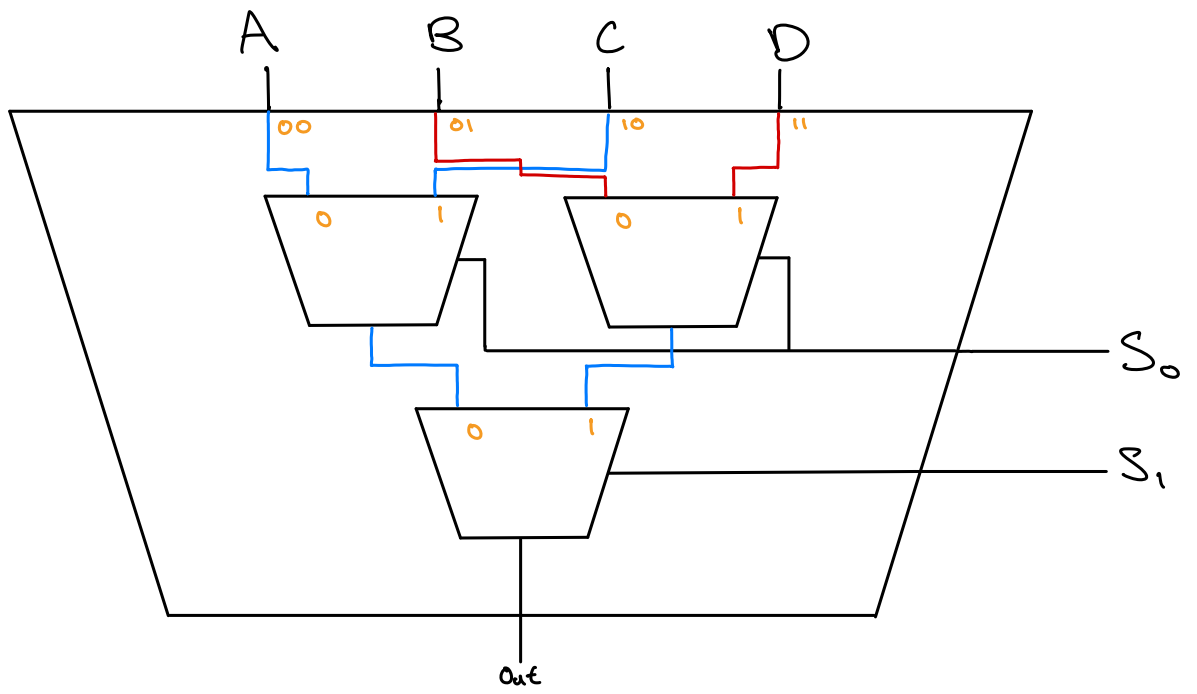

b)

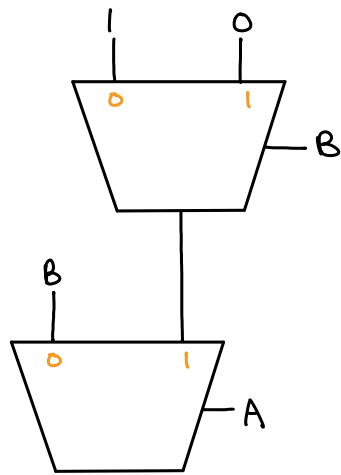

A	B	xOR
0	0	→ 0
0	1	→ 1
1	0	→ 1
1	1	→ 0