
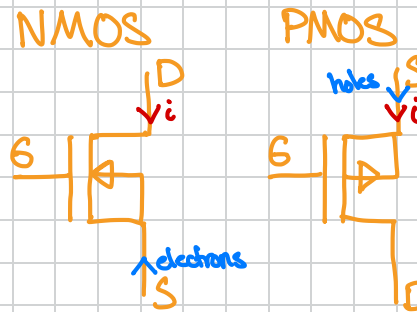




MOSFET REVIEW
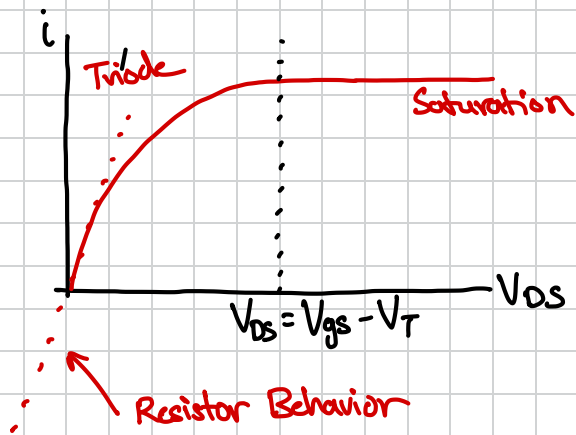
$$i = \mu_n C_{ox} \frac{W}{L} \left[(V_{gs} - V_T) V_{ds} - \frac{V_{ds}^2}{2} \right] \quad \leftarrow \text{NMOS}$$




$$i = \mu_p C_{ox} \frac{W}{L} \left[(V_{sg} - V_T) V_{sd} - \frac{V_{sd}^2}{2} \right] \quad \leftarrow \text{PMOS}$$

DIGITAL INVERTER

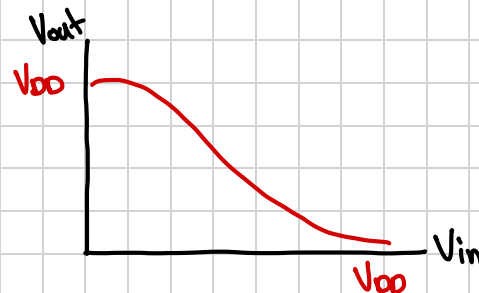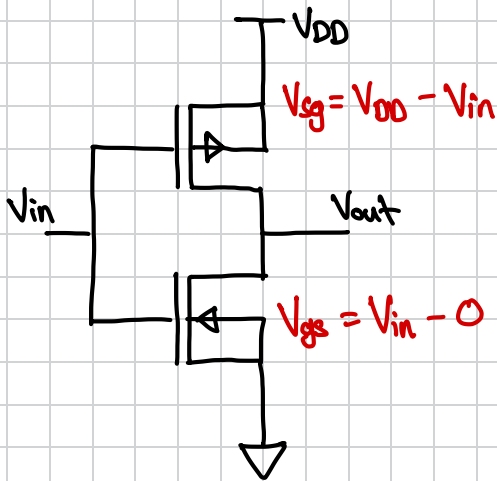

ANALOG CIRCUIT

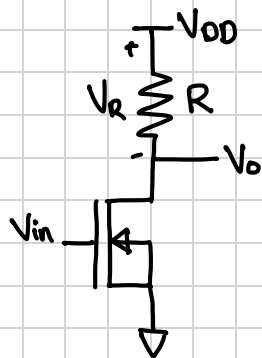

IF MOSFET is in saturation

$$V_o = V_{DD} - V_R$$

$$= V_{DD} - R \times \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_T)^2$$

- Inverting } Properties
- Amplifier }

METHOD OF ASSUMED STATES

AKA. Guess & Check

- ① Guess by plugging in and solving
- ② Check saturation assumptions

$$V_{DS} > V_{GS} - V_T$$