

Finite State Machine

- ① Set of inputs
- ② Set of outputs
- ③ Set of states, one designated initial state
- ④ State transitions
 - └ State transition graph
 - └ state transition table
- ⑤ Output determination



Moore FSM $NS = f(CS, inputs)$

Output = $f(CS)$


Graph (Nodes, Edges)


\Downarrow
 one node/state

\Downarrow
 Transition

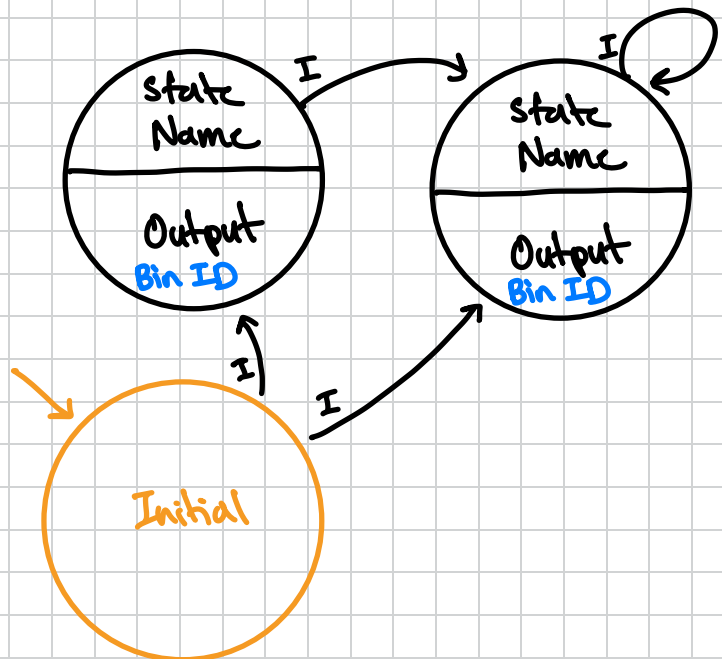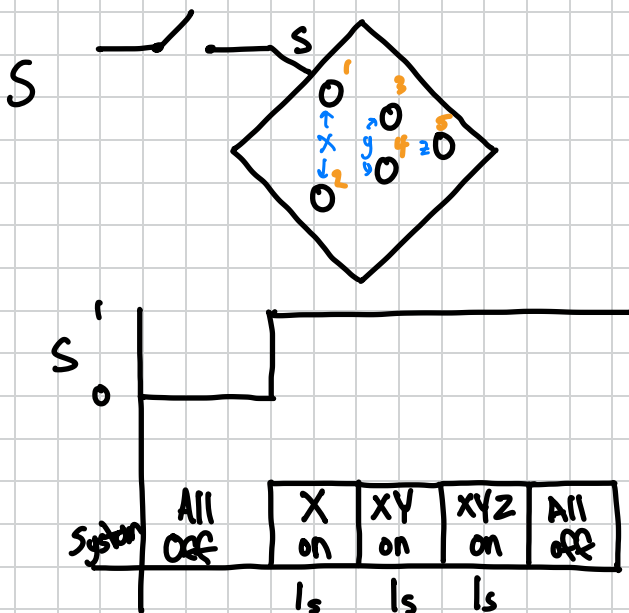


STG

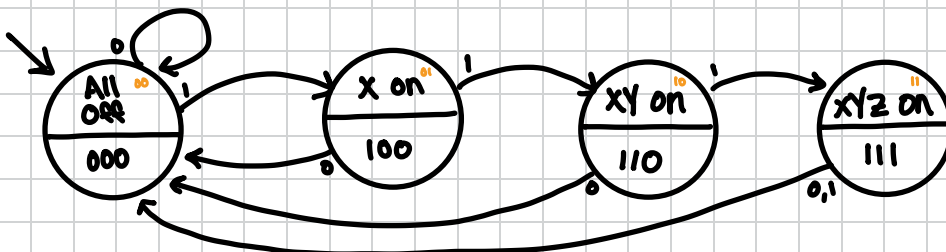

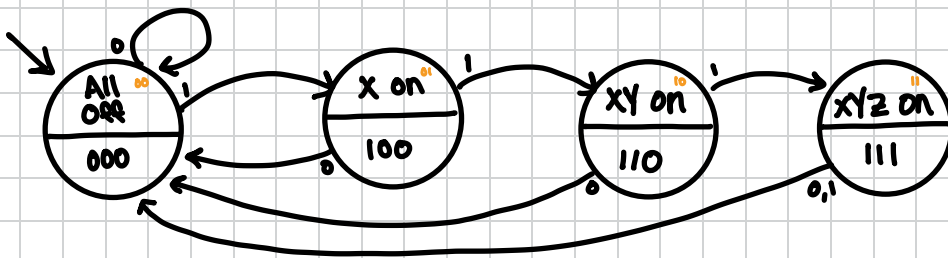


STT (truth table)

	CS		I	NS		Outputs		
	CS ₁	CS ₀	S	NS ₁	NS ₀	X	Y	Z
0	0	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0
2	0	1	0	0	0	1	0	0
3	0	1	1	1	0	1	0	0
4	1	0	0	0	0	1	1	0
5	1	0	1	1	1	1	1	0
6	1	1	0	0	0	1	1	1
7	1	1	1	0	0	1	1	1

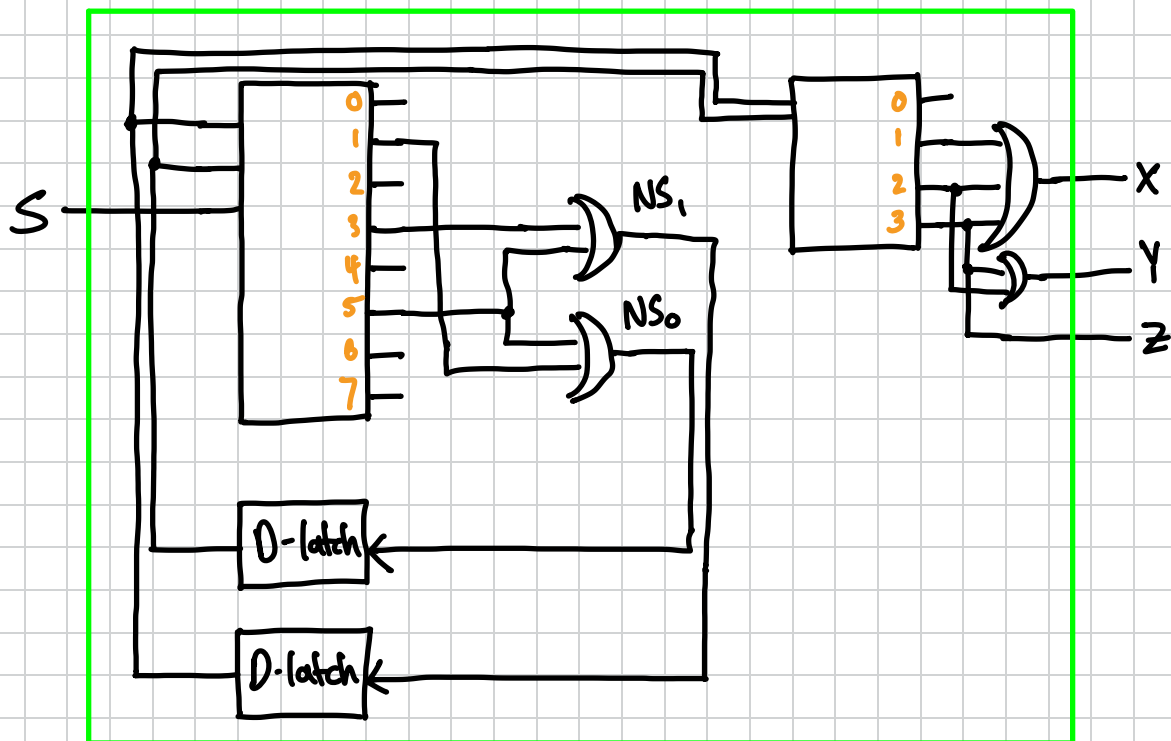


Clock $Q \rightarrow A$

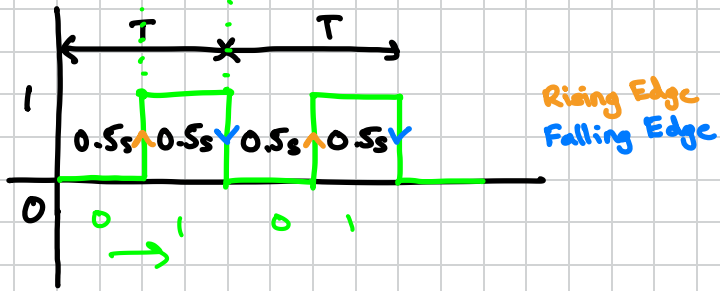

Edge Triggered Latch

D-latch

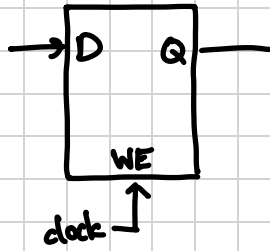

WE							
	X	Y	Z	P	P'	P''	
	P	P	P	P	P'	P''	

Level Triggered Latch

D Flip-Flop

