

Superposition

If a circuit is linear,

Choose $\vec{u}_1 = \begin{bmatrix} u \\ 0 \\ 0 \\ \vdots \end{bmatrix} \rightarrow \vec{y}_1$

Output due to u alone

Choose $\vec{u}_2 = \begin{bmatrix} 0 \\ v \\ 0 \\ \vdots \end{bmatrix} \rightarrow \vec{y}_2$

Output due to v alone


Choose $a, b = 1$

$$\vec{y} = 1 \times \vec{y}_1 + 1 \times \vec{y}_2 + \dots$$

True
Output


Output due
to u alone

Output due
to v alone

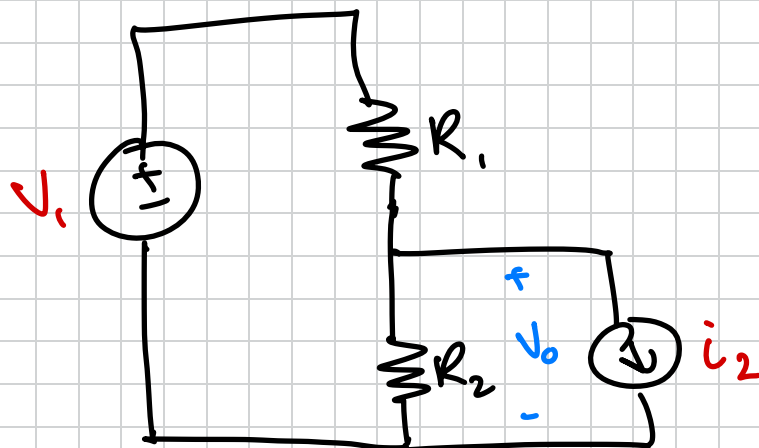

Inputs
Outputs


Apply voltage source alone

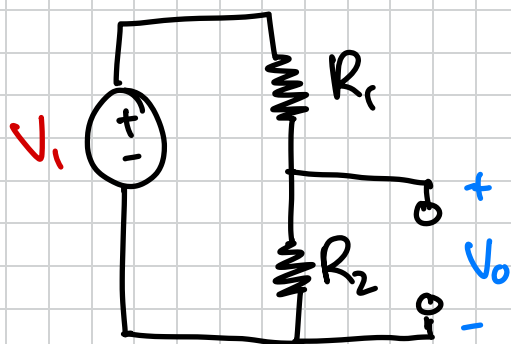

$$V_0 = \frac{R_2}{R_1 + R_2} V_1$$

Output due to V_1 alone


Apply current source alone

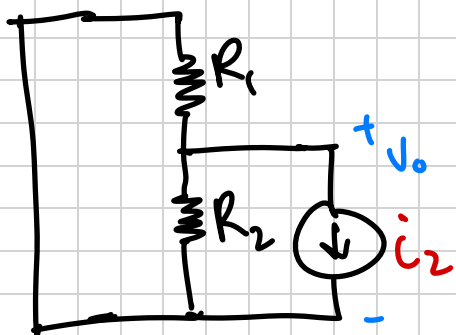

$$V_0 = - \frac{R_1 R_2}{R_1 + R_2} i_2$$

Output due to i_2 alone

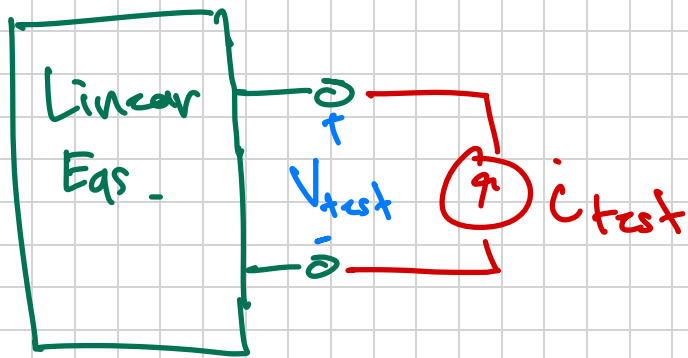
$$V_0 = \frac{R_2}{R_1 + R_2} V_1 - \frac{R_1 R_2}{R_1 + R_2} i_2$$




$$V_{test} = \underbrace{(aV_1 + Ri_2 + \dots)}_{\text{Inside Box}} + \underbrace{R_o \times i_{test}}_{\text{Outside Box}}$$

$$V_{test} = V_{oc} + R_o i_{test}$$

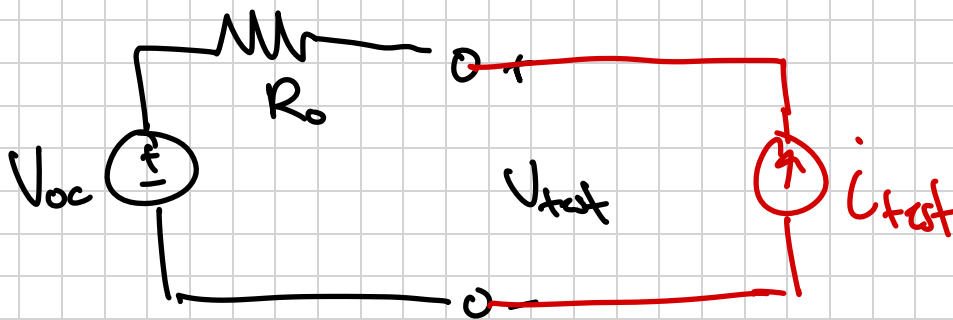Output Resistance
Open Circuit Voltage
 V_{oc}



★ Theremin's Theorem

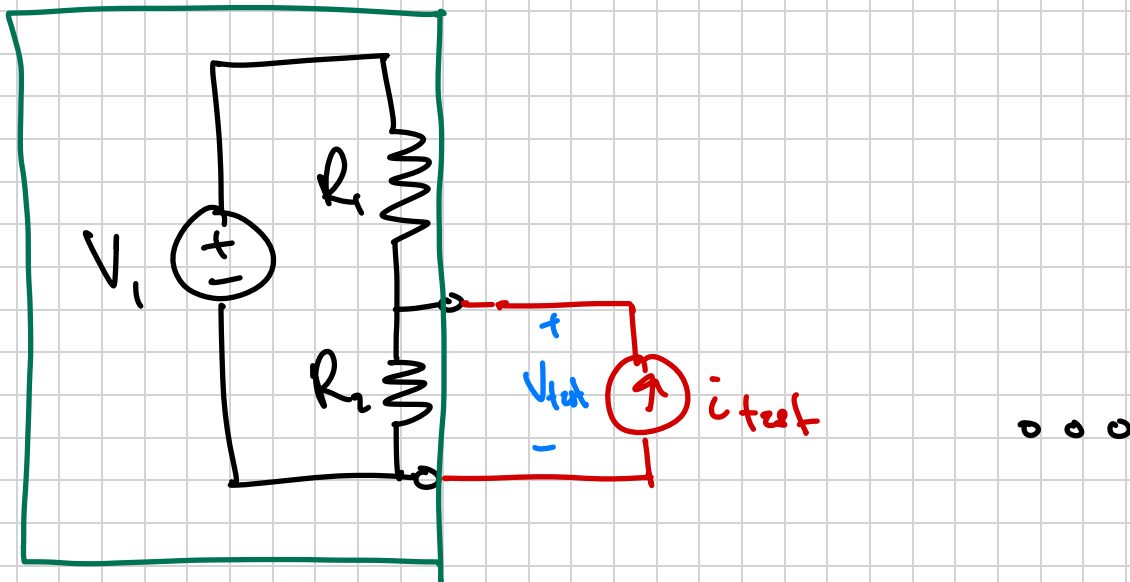

$$V_{test} = \underbrace{\frac{R_2}{R_1 + R_2} V_1}_{V_{oc}} + \underbrace{\frac{R_1 R_2}{R_1 + R_2}}_{R_o} i_{test}$$

