 


# Combinational Logic Circuits

## System

- Requirements



⇒

## Design Solution

① TT inputs outputs

② Logic expressions


PLA

⇓  
simplify


⇓  
circuit! ☆

③


# 1-bit Storage

 

## R-S Latch

 

 D-Latch : Avoids invalid state of an R-S latch by design



| D   | WE |                      |
|-----|----|----------------------|
| 0/1 | 0  | S=1<br>R=1 Holds     |
| 0   | 1  | S=1<br>R=0 Latches 1 |
| 1   | 1  | S=0<br>R=1 Latches 0 |


| D | WE | Q     |
|---|----|-------|
|   | 0  | Holds |
| D | 1  | D     |

# Memory is multi bit storage

4 GiB  $\rightarrow$  Byte 8-bits

Gi - Gibi  
 $2^{30}$

$$4 \cdot 2^{30} = 2^{32}$$

 

4x3 memory

