 



①



S	R	a
0	0	holds
0	1	1 latches
1	0	0 latches
1	1	invalid

2

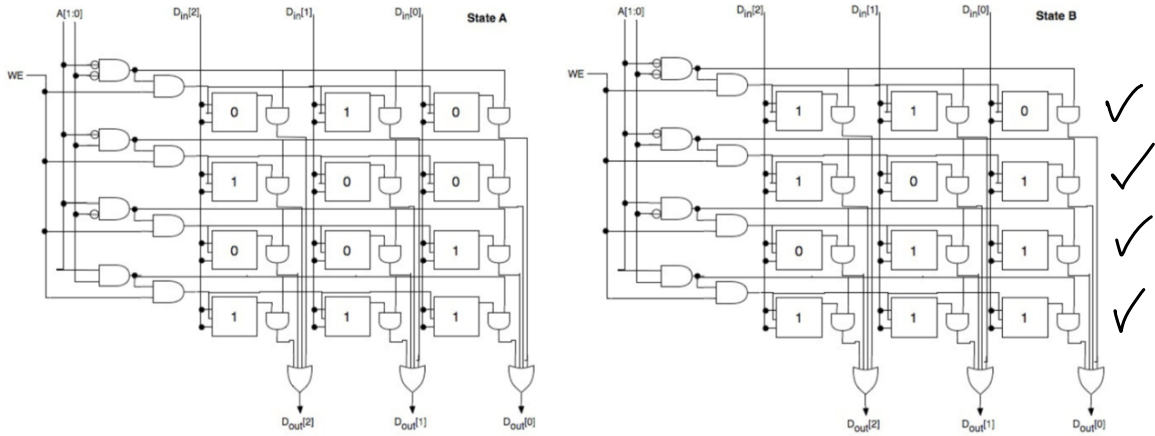2. (10 pts) After five clock cycles memory goes from state A to state B (shown below). The table below shows values of the 2-bit address ($A[1:0]$), 1-bit Write-Enable and 3-bit D_{in} signals. For each cycle, fill in the missing bits (represented by dashes)




	$A[1:0]$		WE	$D_{in}[2:0]$		
Cycle 1	1	0	1	0	1	1
Cycle 2	1	1	0/1	1	1	1
Cycle 3	0	0	1	0	0	0
Cycle 4	0	0	1	1	1	0
Cycle 5	0	1	1	1	0	1

3

Input is the scheduler which can pick one of 3 states, 00, 01, 10.

a.

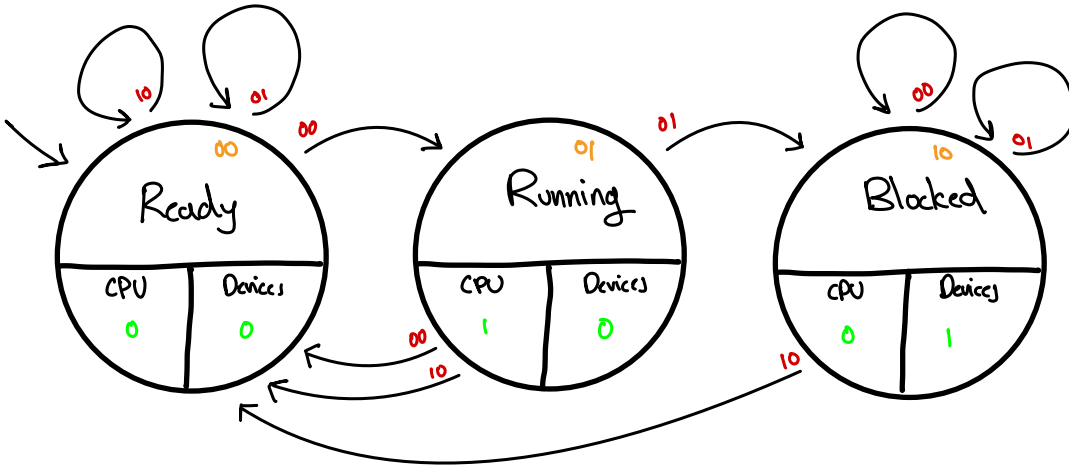

b.


C.S.	I	NS.
0 0	0 0	0 1
0 0	0 1	0 0
0 0	1 0	0 0
0 1	0 0	0 0
0 1	0 1	1 0
0 1	1 0	0 0
1 0	0 0	1 0
1 0	0 1	1 0
1 0	1 0	0 0

c.

C.S.	CPU	Dev
0 0	0	0
0 1	1	0
1 0	0	1

4

a.

 

b. $2^4 = 16$

You would need a $4 \rightarrow 16$ decoder


c. $S_1'S_0' + S_1S_0 = \text{XNOR}(S_1, S_0)$

5

a.

CS, CS ₀		I	NS, NS ₀		X
C.S.			N.S.		
0	0	0	0	0	1
0	0	1	1	0	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	1	0
1	0	1	0	0	0

b.

 


6


a.

C.S.	Out
00	11
01	01
10	10

b.

 

7

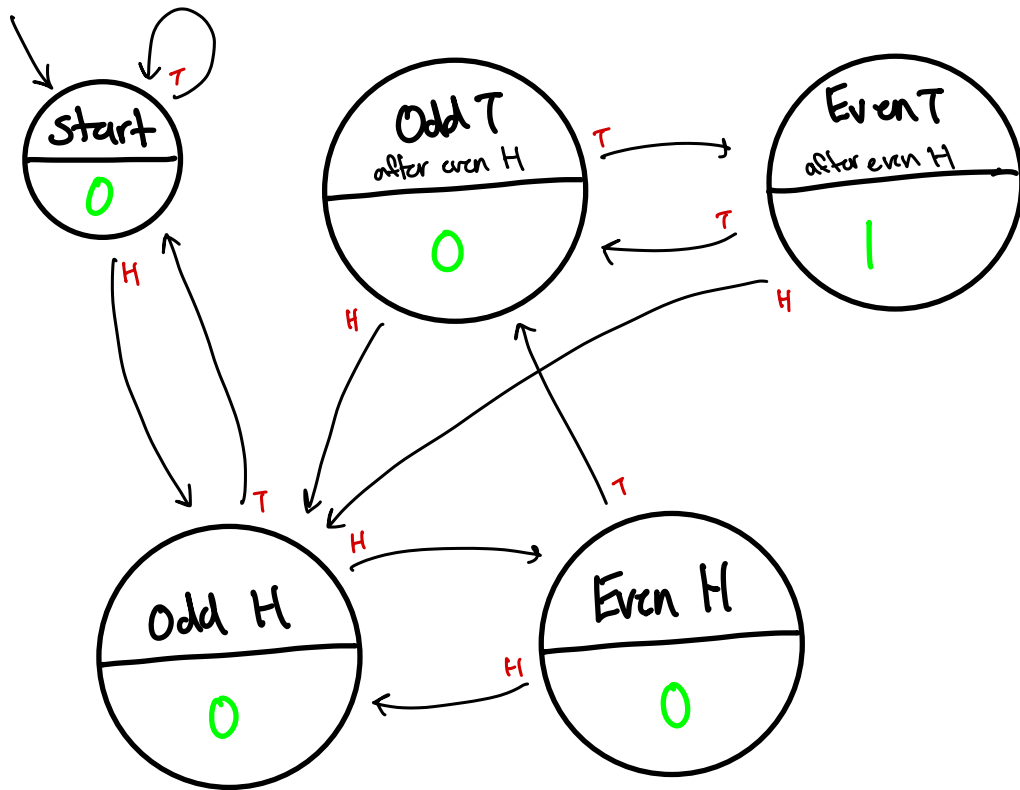

What if not restricted to even T after even H

