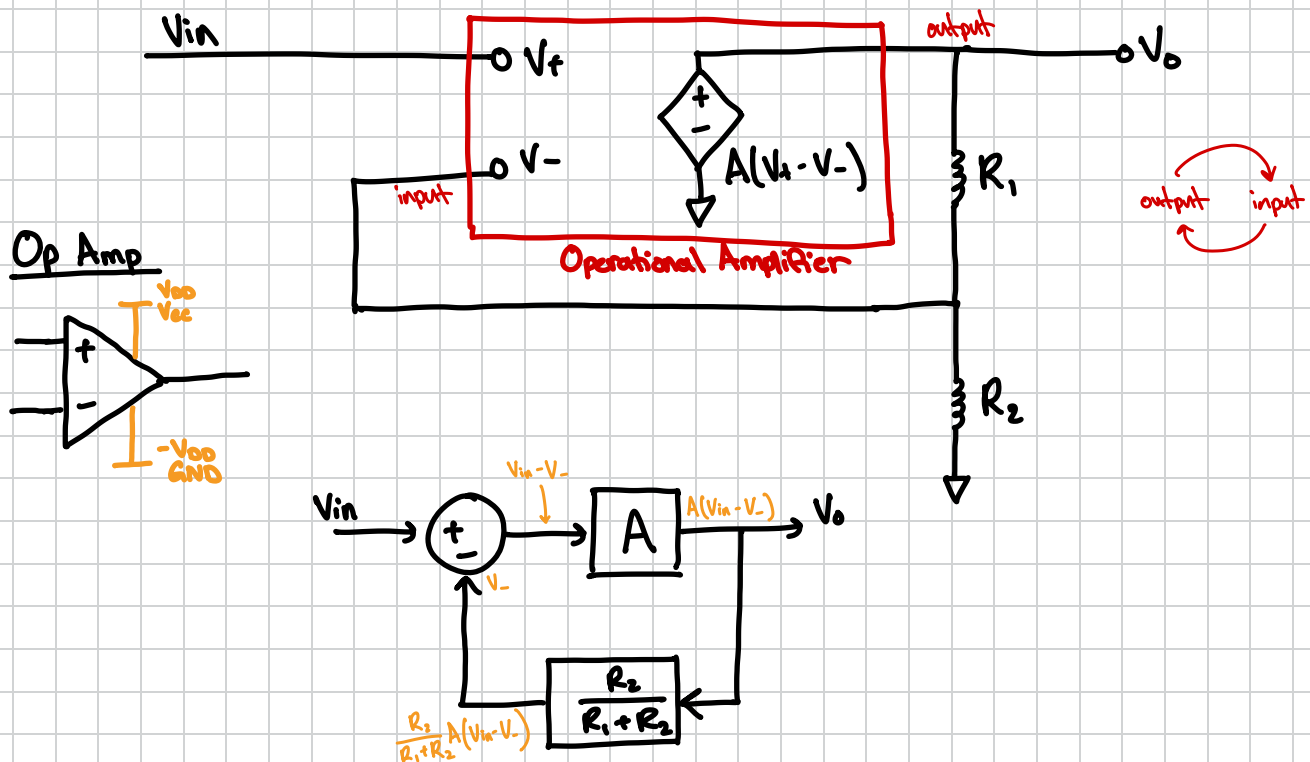


FEEDBACK



$$V_o = A(V_+ - V_-)$$

$$V_o = A\left(V_{in} - \underbrace{\frac{R_2}{R_1 + R_2} V_o}_{\text{Feedback}}\right)$$

$$\left(1 + A \frac{R_2}{R_1 + R_2}\right) V_o = A V_{in}$$

$$V_o = \frac{A^{\text{Gain}}}{1 + A \frac{R_2}{R_1 + R_2}} V_{in}$$

$$\approx \frac{R_1 + R_2}{R_2} V_{in}$$

$$V_- \rightarrow V_{in} = V_+$$

★ No new tools yet

Let $A \rightarrow \infty$
Let $A \gg \frac{R_1 + R_2}{R_2}$

Golden Rule of Negative Feedback

- 1) if negative feedback
- 2) if $A \rightarrow \infty$
- 3) if stable

$$\Rightarrow V_+ - V_- = 0 \quad \boxed{V_- = V_+}$$

