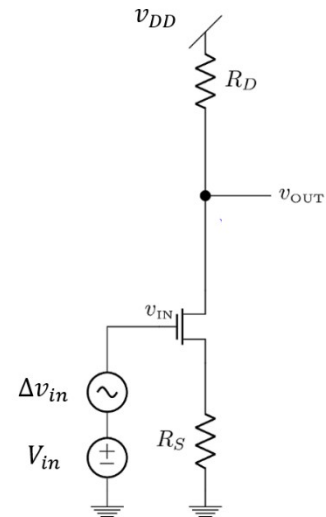


Part I

Q1

Consider the circuit at right, consisting of an NMOS transistor and two resistors. The supply voltage  $v_{DD}$ , shown as a bar at the top of the circuit, is supplied by a constant voltage source from ground (not shown). The input has a constant voltage  $V_i$  and is to be perturbed by an amount  $\Delta v_i$ ; this is shown pictorially as two voltage sources in series. You may use the transconductance,  $g_m = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_T)$ , as a known quantity. Assume that the MOSFET is in the saturation region.



**[a=6pt]** Consider the circuit with  $R_S \rightarrow 0$  and calculate the small-signal gain of the amplifier,  $\Delta v_{out} / \Delta v_i$ .

$$V_o = -R_D g_m \Delta V_{gs} = \underline{-g_m R_D V_{in}}$$

**[b=3pt]** The transconductance is very large but poorly controlled and may vary by up to a factor of 2 from circuit to circuit. If this were to happen, by what factor would the small-signal gain vary when  $R_S \rightarrow 0$  as in (a)?

$$\times 2$$

**[c=7pt]** Consider the circuit again with  $R_S \neq 0$  and calculate the small-signal gain of the amplifier,  $\Delta v_{out} / \Delta v_i$ .

$$\Delta V_o = -\Delta i R_D = \frac{-g_m R_D}{1 + g_m R_S} \Delta V_{in}$$

**[d=3pt]** Consider the transconductance to be very large. Using the result from (c) where  $R_s \neq 0$ , by what factor would the small-signal gain vary if  $g_m$  varied by a factor of 2?

Even if  $g_m$  varies by  $\times 2$   
 $\frac{\Delta V_o}{\Delta V_i}$  won't change.

**[e=6pt]** Finally, consider that the power supply may have some perturbation such that  $v_{DD} = V_{DD} + \Delta v_{DD}$ . With no other perturbations in the circuit, calculate the Power Supply Rejection Ratio, i.e.  $\Delta v_{DD} / \Delta v_{out}$ .

$$\boxed{\frac{\Delta v_{dd}}{\Delta V_o} = 1.}$$

This circuit provides no rejection of power supply disturbances.

Q2

[a=5pt] Prove de Moivre's formula, which states that  $(\cos \theta + j \sin \theta)^n = \cos n\theta + j \sin n\theta$

$$(\cos \theta + j \sin \theta)^n = (e^{j\theta})^n = e^{jn\theta} = \cos n\theta + j \sin n\theta$$

[b=5pt] Use de Moivre's formula from part (a) to prove the trigonometric "double-angle" identities, namely

$$\begin{aligned}\cos 2\theta &= \cos^2 \theta - \sin^2 \theta \\ \sin 2\theta &= 2 \cos \theta \sin \theta\end{aligned}$$

[Note that you may use de Moivre's formula for part (b) whether you proved it in part (a) or not]

$$\begin{aligned}(\cos \theta + j \sin \theta)^2 &= (\cos^2 \theta - \sin^2 \theta) + j 2 \cos \theta \sin \theta \\ &= \cos 2\theta + j \sin 2\theta \\ \Rightarrow \cos 2\theta &= \cos^2 \theta - \sin^2 \theta \\ \sin 2\theta &= 2 \cos \theta \sin \theta\end{aligned}$$

[c=5pt] Consider a particular transfer function  $T$  below. Express  $T$  in polar **and** rectangular coordinates.

$$T = \frac{3+4j}{12-5j}$$

$$0.385 e^{j75.75^\circ}$$


$$0.0947 + 0.373j$$

[d=5pt] On a logarithmic number line, what number falls exactly halfway between 1 and 10?

$$\sqrt{10} = 3.162$$

[e=5pt] A filter has a transfer function  $\frac{V_o}{V_i}$  as given in the figure (the frequency axis is in Hz).

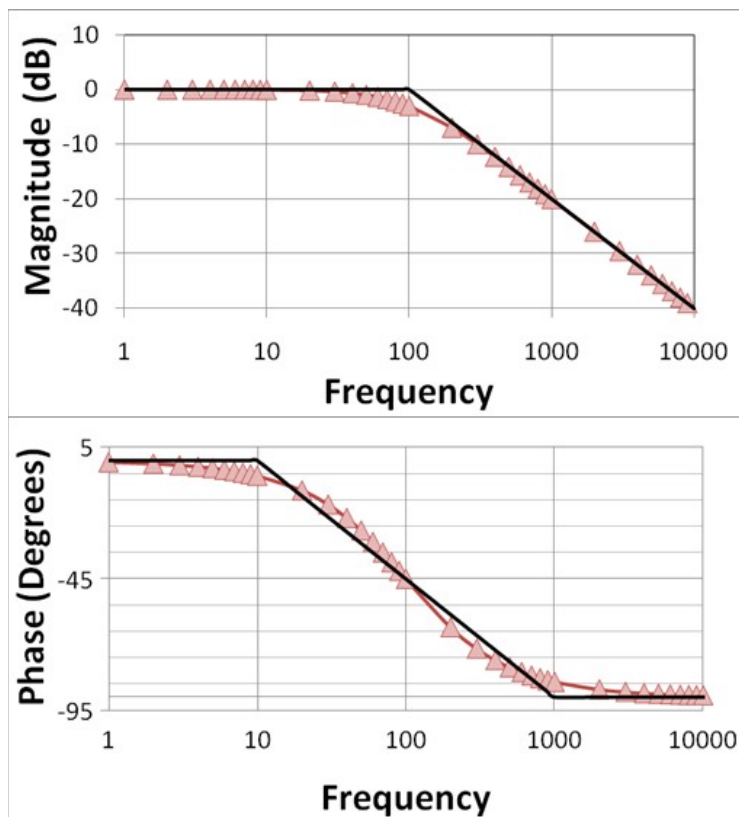The input voltage is a cosine wave at 1 kHz with amplitude 3 and a phase of 20 degrees. What will the frequency, amplitude, and phase of the output voltage be?



$$Amp = 0.3$$

$$\text{Output phase} = 20 - 85$$
$$= -65^\circ$$

Part II

Q3

$$(a) V_{in}(t) = 10 \cos(2 \times 10^6 t + 45^\circ) \text{ V}$$

$$V_{in} = 10 e^{j45^\circ} \text{ V}$$

$$(b) Z_R = R = 1 \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 2 \times 10^6 \times 0.25 \times 10^{-6}} = -2j \Omega$$

$$(c) \frac{V_{out1}}{V_{in}} = \frac{Z_R}{2Z_R + Z_C} = \frac{1}{2 - 2j} = \frac{1}{4}(1+j)$$

$$\frac{V_{out2}}{V_{in}} = \frac{Z_C}{2Z_R + Z_C} = \frac{-2j}{2 - 2j} = \frac{1}{2}(1-j)$$

$$(d) I = \frac{V}{Z} = \frac{10 e^{j45^\circ}}{2 - 2j} = \frac{10 e^{j45^\circ}}{2\sqrt{2} \cdot e^{j-45^\circ}} = \frac{5}{\sqrt{2}} e^{j90^\circ}$$

$$I(t) = 3.535 \cos(2 \times 10^6 t + 90^\circ)$$

$$(e) \omega \rightarrow \infty, Z_C \rightarrow 0.$$

$$|V_{out1}| = \frac{1}{2} |V_{in}| = 5 \text{ V}$$

$$|V_{out2}| = 0 \text{ V}$$


## Part 2



Q1


Answer to parts (i), (ii), (iii)

```
Cutoff frequency : 159154.94 Hz
Input signal period : 0.001 s
Input DC component : 0.2 V
Input phasor component 1 magnitude: 0.37419571351545566 V
Input phasor component 1 phase: 0 degrees
Input phasor component 2 magnitude: 0.3027306914562628 V
Input phasor component 2 phase: 0 degrees
Input phasor component 3 magnitude: 0.2018204609708419 V
Input phasor component 3 phase: 0 degrees
Input phasor component 4 magnitude: 0.09354892837886393 V
Input phasor component 4 phase: 0 degrees
Output DC component : 0.2 V
Output phasor component 1 magnitude: 0.37418832740682695 V
Output phase component 1 phase: -0.3599952627020996 degrees
Output phasor component 2 magnitude: 0.30270679162948966 V
Output phase component 2 phase: -0.7199621043095835 degrees
Output phasor component 3 magnitude: 0.2017846165363827 V
Output phase component 3 phase: -1.0798721171883547 degrees
Output phasor component 4 magnitude: 0.09351939705903721 V
Output phase component 4 phase: -1.4396969206094188 degrees
```

Plots for part (iv)

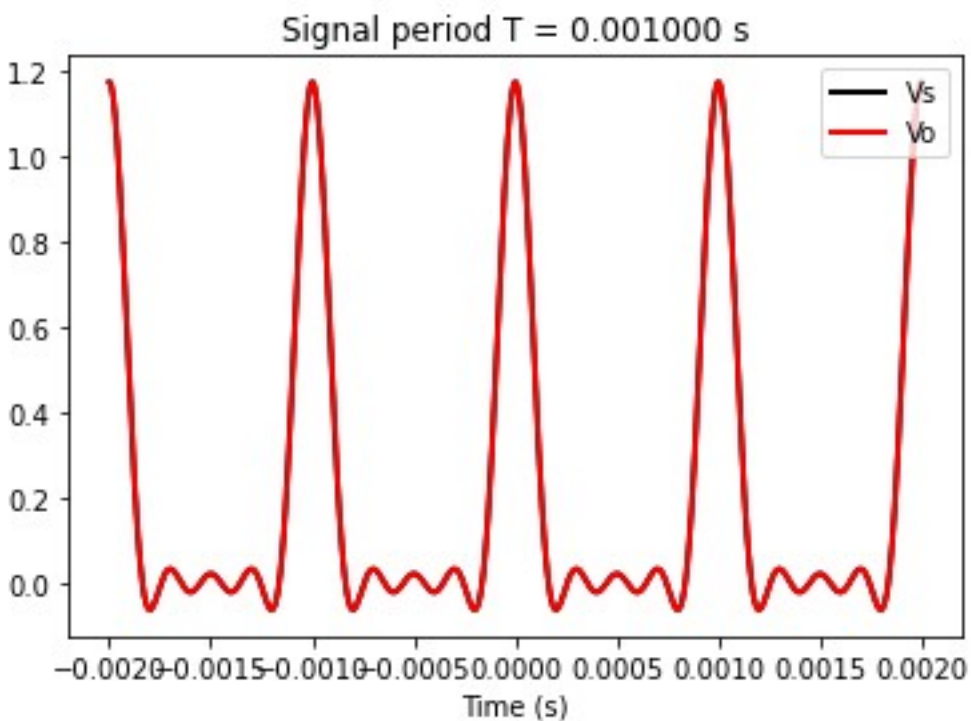

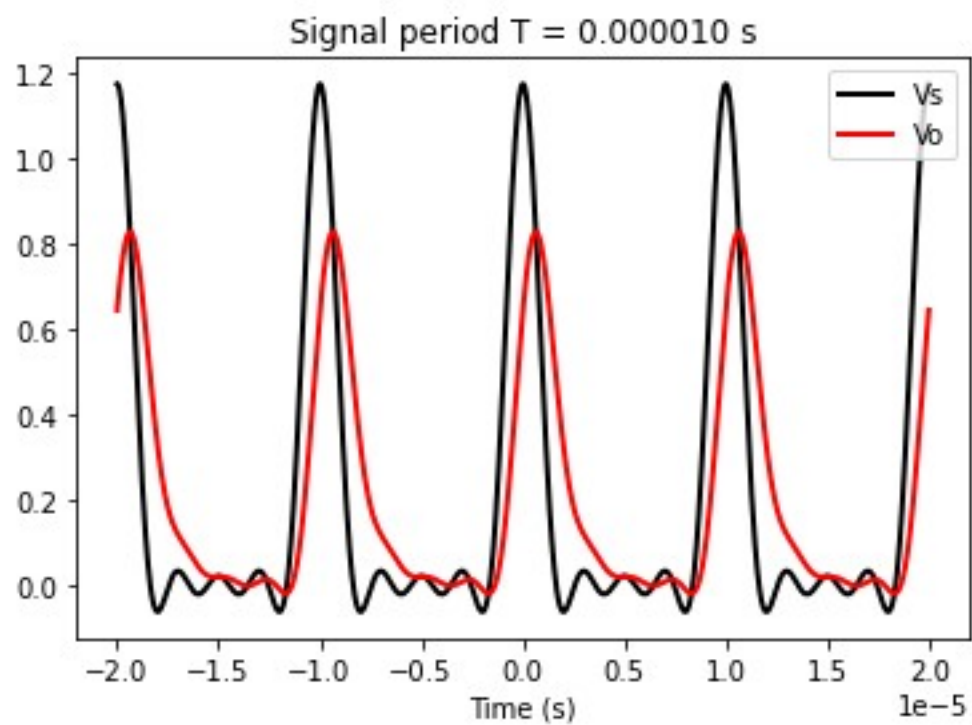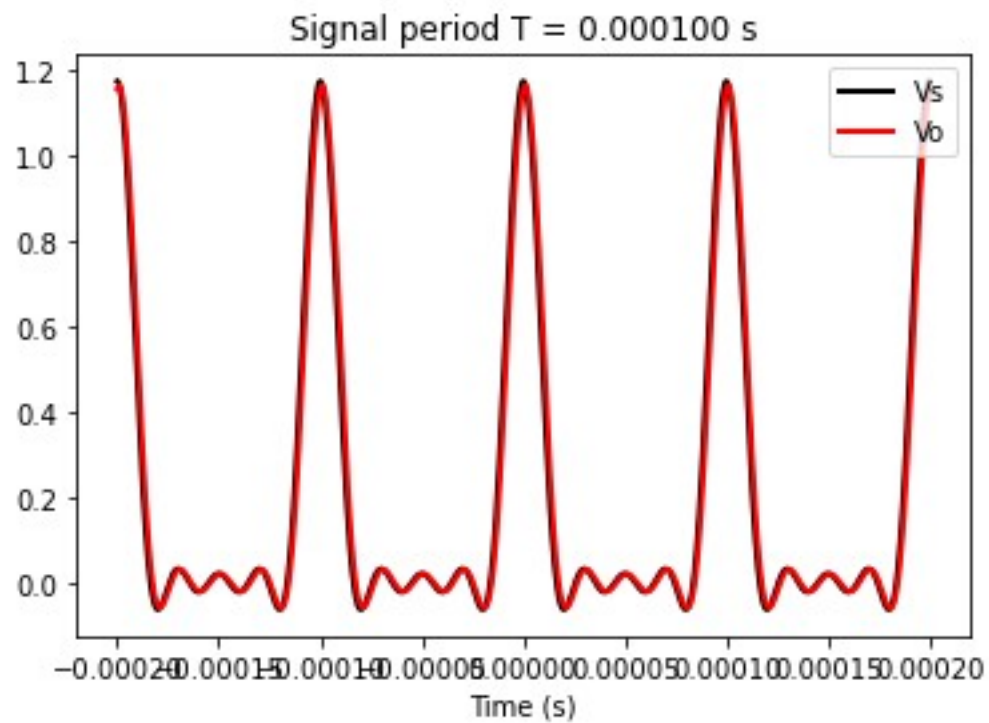

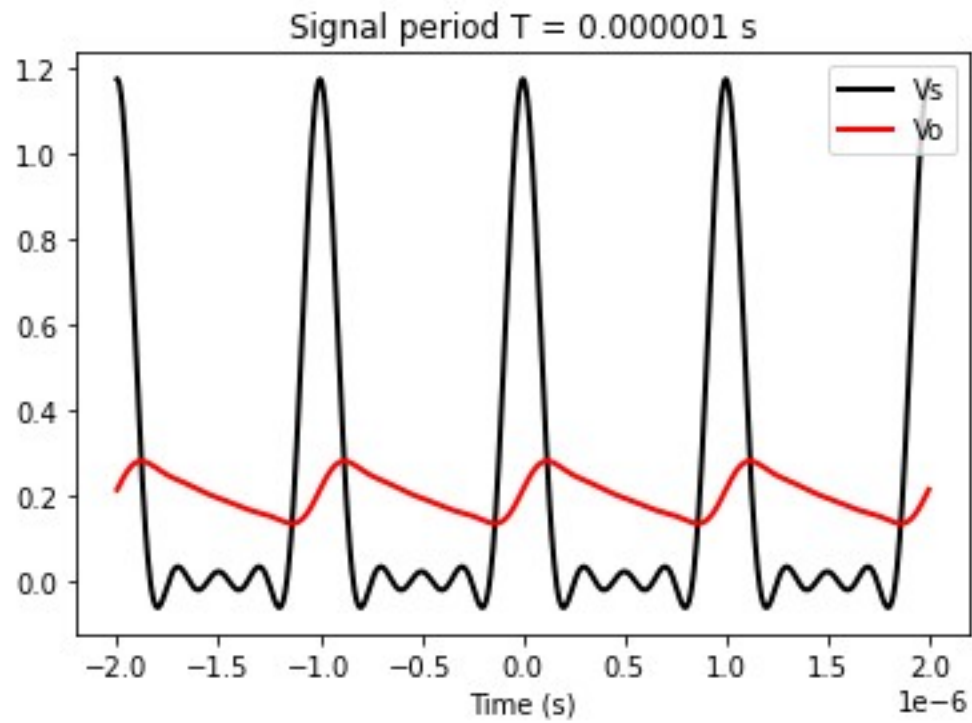


Q2

$$(a) \frac{R + j\omega[L - R^2C + \omega^2 R^2 LC^2]}{1 + \omega^2 R^2 C^2}$$


$$(b) \left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\left[ (1 - \omega^2 LC)^2 + \left( \frac{\omega L}{R} \right)^2 \right]^{1/2}}$$

(c), (d), (e)

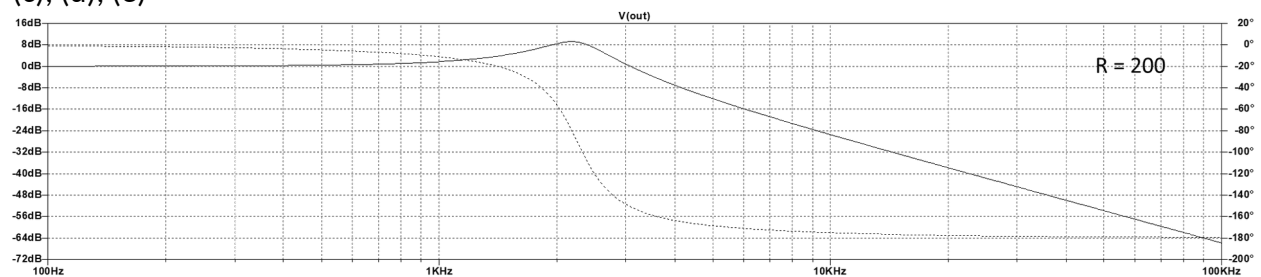





R = 50

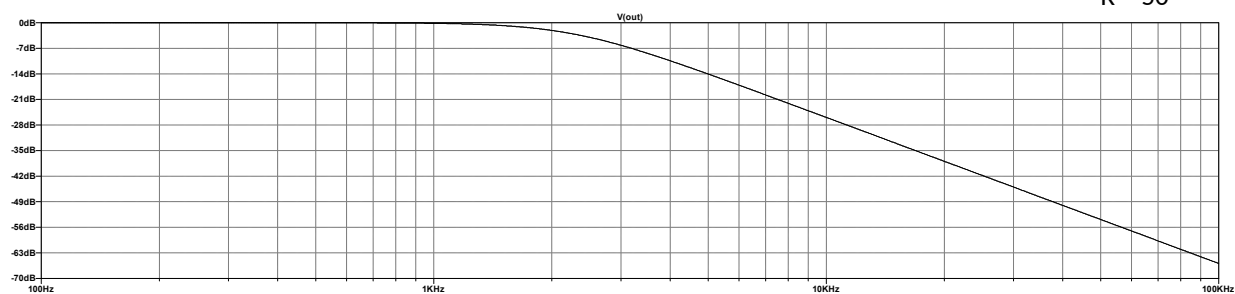


R = 100

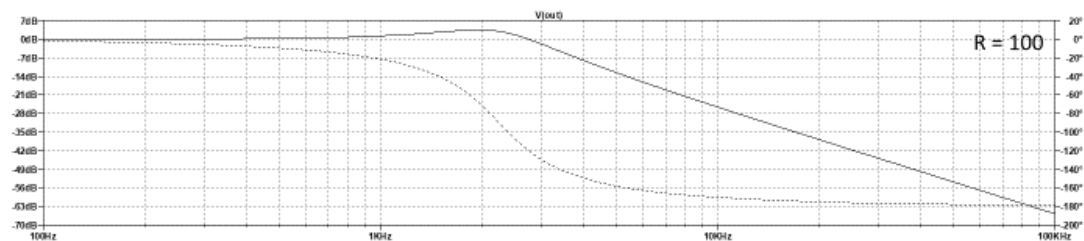


R = 300

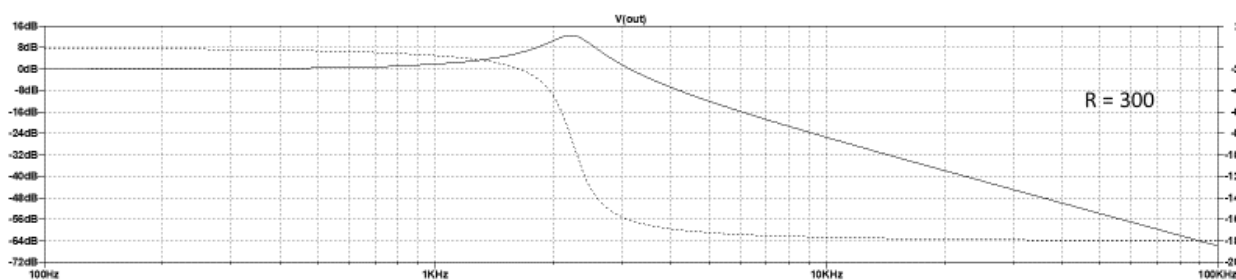

R = 100 k

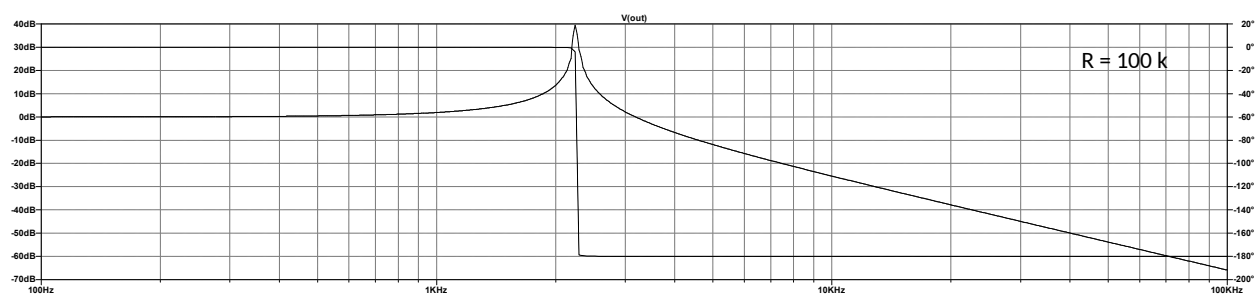

Resistor removed. ( $R = \infty$ )

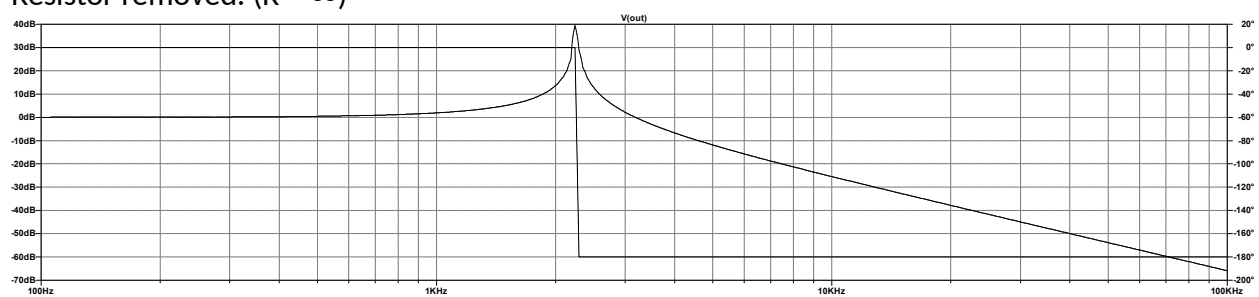

| R (Ohms)         | f0 (kHz) | VMAX from LTSPICE (dB) |
|------------------|----------|------------------------|
| 100k or $\infty$ | 2.23     | 39.39                  |
| 300              | 2.23     | 12.59                  |
| 200              | 2.18     | 9.16                   |
| 100              | 1.99     | 3.57                   |
| 50               | -        | 0                      |

(f) If the resistor value is below about 300 Ohms, the resonance frequency (peak VOUT response) starts to reduce; simultaneously, the peak value of VOUT drops. When R = 50 Ohms, there is no observable resonance and we can conclude the circuit is no longer resonant. As R increases above 100 Ohms, the peak voltage VOUT increases and saturates at ~ 40 dB, which is also the peak value for the LC circuit (with R removed).