
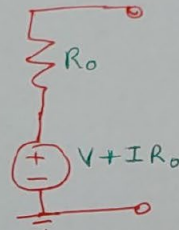


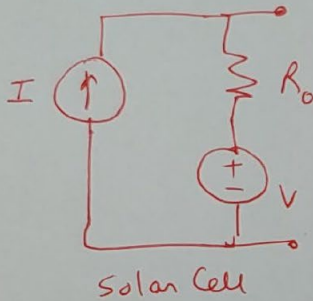
Q3

Solution.

It helps to find the Thevenin & Norton Equivalents for a solar cell




Thevenin Eq. (use superposition)

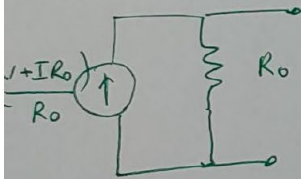

Norton Equivalent

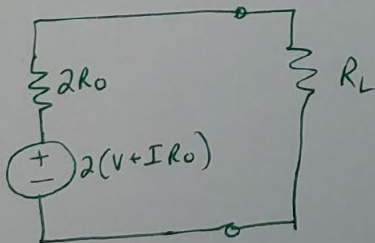
(a) Combine 2 cells in series (use Thevenin Eqs) and add to voltage across  $R_L$



$$= 2(V + IR_o) \left( \frac{R_L}{R_L + 2R_o} \right)$$

$$= \frac{2(V + IR_o) R_L}{(R_L + 2R_o)}$$

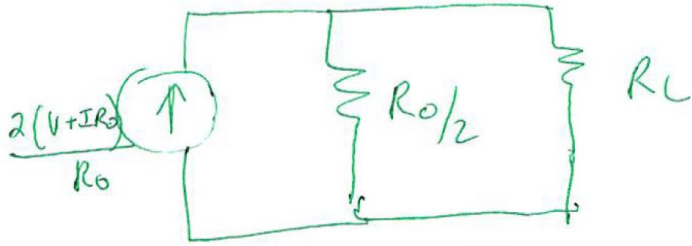(b) Combine 2 cells in parallel. (use Norton eq)



current through  $R_L$

$$= \frac{2(V + IR_0)}{R_0} \left( \frac{R_0/2}{R_0/2 + R_L} \right)$$

$$= \frac{2(V + IR_0)}{\cancel{R_0}} \left( \frac{\cancel{R_0}}{R_0 + 2R_L} \right)$$

$$= \frac{2(V + IR_0)}{R_0 + 2R_L}$$