

RC CIRCUIT

$$RC \frac{dv_c}{dt} + v_c = v_{in}$$

$$v_{in}(t) = V_{in} \cos(\omega t) = \operatorname{Re} \{ V_{in} e^{j\omega t} \}$$
$$v_c(t) = V_c \cos(\omega t + \phi) = \operatorname{Re} \{ V_c e^{j(\omega t + \phi)} \} = \operatorname{Re} \{ V_c e^{j\omega t} e^{j\phi} \}$$

↑ unknown

$\operatorname{Re} \{ \}$ disappear

$$\left(\frac{d}{dt} \right)^n \Rightarrow \times (j\omega)^n$$

$$RC(j\omega) V_c e^{j\phi} + V_c e^{j\phi} = V_{in} e^{j0}$$

$$\boxed{\frac{V_c}{V_{in}}} = \frac{V_c e^{j\phi}}{V_{in} e^{j0}} = \boxed{\frac{1}{1 + j\omega RC}} \quad \begin{array}{l} \text{Transfer} \\ \text{Function} \end{array}$$

$$RC V_c \cancel{e^{j\omega t}} e^{j\phi} j\omega + V_c \cancel{e^{j\omega t}} e^{j\phi} = V_{in} \cancel{e^{j\omega t}}$$

$$V_c e^{j\phi} (RC j\omega + 1) = V_{in} e^{j0}$$

$$\frac{V_c e^{j\phi}}{V_{in} e^{j0}} = \frac{1}{1 + RC j\omega}$$


$$\text{find } \frac{V_c}{V_{in}} = |TF| = \left| \frac{V_c}{V_{in}} e^{j\phi} \right| = \left| \frac{V_c}{V_{in}} \right| |1 e^{j\phi}| = \frac{V_c}{V_{in}}$$

$$\left| \frac{1}{1 + RCj} \right| = \frac{|1|}{|1 + RCj\omega|} = \frac{1}{\sqrt{1 + (\omega RC)^2}} \quad \star \text{ Gain}$$

$$\text{find } \phi = \angle TF$$


$$\angle \frac{1}{1 + RCj\omega} = \frac{1}{M e^{j \arctan(\omega RC/1)}} = M e^{j \underbrace{[-\arctan(\omega RC)]}_{\phi}}$$

CAPACITOR FREQUENCY DOMAIN

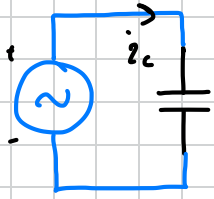


$$\begin{aligned} i_c &= C \frac{dv_c}{dt} \\ I_c e^{j\phi} &= C j\omega V_c e^{j\phi} \\ \vec{i}_c &= j\omega C \vec{v}_c \\ \vec{v}_c &= \underbrace{\left(\frac{1}{j\omega C}\right)}_{\text{impedance } Z_c} \vec{i}_c \end{aligned}$$


IMPEDANCE SOLUTION

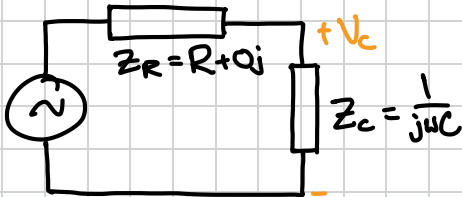


$$\vec{v}_c = \frac{Z_c}{Z_R + Z_c} \vec{v}_{in} = \frac{1/j\omega C}{R + 1/j\omega C} \vec{v}_{in} = \frac{1}{j\omega RC + 1} \vec{v}_{in}$$

RLC

Resistor: $v = Ri$ $\vec{v} = R\vec{i}$ $Z_R = R$ 

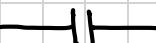Capacitor: $i = C \frac{dv}{dt}$ $\vec{v} = \frac{1}{j\omega C} \vec{i}$ $Z_C = \frac{1}{j\omega C}$ 

Inductor: $v = L \frac{di}{dt}$ $\vec{v} = j\omega L \vec{i}$ $Z_L = j\omega L$ 



$$\begin{aligned}\vec{i} &= \frac{1}{Z_R + Z_L + Z_C} \vec{V}_{in} \\ &= \frac{1}{R + j\omega L + \frac{1}{j\omega C}} \vec{V}_{in} \\ &= \frac{j\omega C}{j\omega RC + (1 - \omega^2 LC)} \vec{V}_{in}\end{aligned}$$

$$\vec{V}_C = Z_C \times i = \frac{1}{j\omega C} \times \frac{j\omega C}{(1 - \omega^2 LC) + j\omega RC} \vec{V}_{in} = \frac{1}{(1 - \omega^2 LC) + j\omega RC} \vec{V}_{in}$$

$$\left| \frac{\vec{V}_C}{\vec{V}_{in}} \right| = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$