



Introduction to Electrical Engineering (ECE 302H) – Homework 7

Dawson Zhang | Instructor: Dr. Hanson

Fall 2025

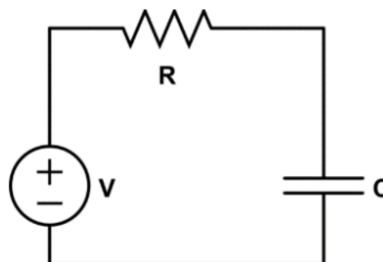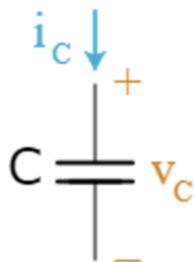Problem 7.1. Capacitors in Circuits

In class, we mainly learned about capacitors in terms of the charge-voltage relationship, $Q = CV$. This becomes a new circuit component for us. In the circuits context, as usual, we focus on it's current- voltage relationship, $i = C \frac{dV}{dt}$.



- Write the KVL, KCL, and component law equations that define how this circuit works (as usual)
- Combine the equations into a single equation in which v_c is the only unknown (as usual)
- Your equation will be a differential equation, which is different from the algebraic equations we've seen so far. Let $V = 0$ and solve the differential equation assuming that the capacitor's voltage starts at V_{ic} . Write a phrase/sentence stating how the capacitor's **initial condition** enters into the calculation.
- Your solution will rely on the product $R \times C$. What are the units of RC ? What is the significance of this number, known as the time constant of the system?
- Create a table with the percent of the overall transition that the capacitor voltage has completed after N time constants, where $N = 1, 2, 3, 4, 5$.
- Use Thevenin's Theorem to demonstrate that a system with a single capacitor (plus any number of resistors and sources) will result in the same solution as above and therefore will be characterized by a single time constant. Do the sources affect the time constant?
- Use LTSpice to simulate the RC circuit with $V = 0\text{ V}$, $R = 10\ \Omega$, $C = 3\ \mu\text{F}$. Label the node below the capacitor as ground and the node above the capacitor as "vc." Place a "spice directive" anywhere on the schematic that says ".ic V(vc)=5" to set the initial condition on the capacitor. Use a transient simulation and make sure to simulate for a long enough time to see the whole transition but not so long of a time that you can't see the transition. Include a screenshot of the schematic and the capacitor voltage as your solution to this part.

Solution.

□

a) KVL:

$$\sum V = V - v_R - v_c = 0$$

KCL:

$$\sum i = i_R - i_c = 0$$

Component Laws:

$$v_R = i_R R$$

$$i_c = C \frac{dv_c}{dt}$$

b)

$$\frac{V - v_c}{R} = C \frac{dv_c}{dt}$$

$$\frac{v_c}{R} + C \frac{dv_c}{dt} = \frac{V}{R}$$

c)

$$\frac{v_c}{R} + C \frac{dv_c}{dt} = \frac{V}{R}$$

$$\frac{v_c}{R} + C \frac{dv_c}{dt} = 0$$

$$C \frac{dv_c}{dt} = -\frac{v_c}{R}$$

$$\frac{RC}{v_c} dv_c = -dt$$

$$\int \frac{RC}{v_c} dv_c = \int -dt$$

$$RC \ln |v_c| = -t + C$$

Here the initial condition enters the equation to solve for C ,

$$RC \ln V_{ic} = 0 + C$$

$$RC \ln V_{ic} = C$$

$$RC \ln |v_c| = -t + C$$

$$RC \ln |v_c| = -t + RC \ln V_{ic}$$

$$\ln |v_c| = -t/RC + \ln V_{ic}$$

$$e^{\ln |v_c|} = e^{-t/RC + \ln V_{ic}}$$

$$v_c = V_{ic} e^{-t/RC}$$

d) Resistance has units of V/A while capacitance has units of A · s/V. Multiplying the two yields s. This number is significant because it controls the rate at which v_c changes.

e)

$$v_c = V_{ic} e^{-N}$$

$$v_{\text{initial}} = V_{ic}$$

$$v_{\text{final}} = 0$$

$$\% \text{ transition} = \frac{V_{ic} - V_{ic} e^{-N}}{V_{ic} - 0}$$




$$\% \text{ transition} = 1 - e^{-N}$$

N	$1 - e^{-N}$	% Complete
1	0.6321	63.2%
2	0.8647	86.5%
3	0.9502	95.0%
4	0.9817	98.2%
5	0.9933	99.3%

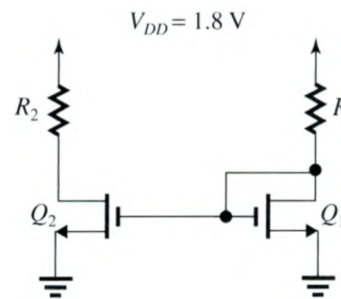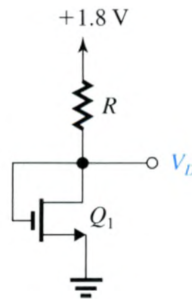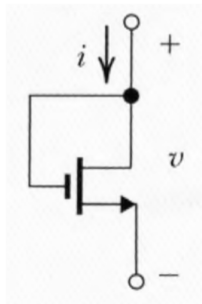Problem 7.2. Diode-Connected Device

Sometimes NMOS transistors have their gates shorted to their drains as shown in the Figure. This is known as a diode connected device.

- Will the transistor operate in the cutoff, linear, or saturation region?
- Assume the MOSFET parameters and geometry (μ_n, C_{ox}, V_t, W, L) are known and ignore channel length modulation ($\lambda = 0$). Calculate the I-V characteristic of this two-terminal device when v is positive and when v is negative. In what way is this characteristic similar to the exponential behavior of a diode and in what way is it not similar?
- The NMOS transistor in the second Figure have $V_t = 0.5\text{ V}$, $\mu_n C_{ox} = 400\text{ }\mu\text{A/V}^2$, $\lambda = 0$, $W = 0.72\text{ }\mu\text{m}$, and $L = 0.18\text{ }\mu\text{m}$. Find the value of R that results in $V_D = 0.7\text{ V}$.
- The third Figure is obtained by augmenting the second Figure with a transistor Q_2 identical to Q_1 but with $W = 2.16\text{ }\mu\text{m}$. As long as Q_2 is in the saturation region, what will I_{D2} be? Does it matter what value R_2 is?
- What value of R_2 results in Q_2 being at the edge of saturation? Should R_2 be bigger or smaller than this value to keep Q_2 in saturation?



Solution.

□

- a) The transistor can be in one of the three states of cutoff, linear, or saturation. Because the gate is shorted to the drain on the NMOS transistor, $V_{DS} = V_{GS} = v$.

Pinch-off occurs at,

$$\begin{aligned} V_{DS} &= V_{GS} - V_T \\ v &= v - V_T \\ V_T &= 0 \end{aligned}$$

That means that the saturation condition becomes if $V_T \geq 0$.

And the linear condition becomes if $V_T < 0$.

Cutoff happens when $v < V_T$.

Assuming this is a normal MOSFET with $V_T \geq 0$, it will be in saturation unless it cutoffs at $v < V_T$.

b)

$$i(v) = \begin{cases} 0, & v < V_T(\text{cutoff}) \\ \frac{1}{2}\mu_n C_{ox} \frac{W}{L} (v - V_T)^2, & v \geq V_T(\text{saturation}) \end{cases}$$

This is similar to a diode because it's a two terminal element with a threshold and strongly nonlinear increase in current.

This is different from a diode because it's quadratic and not exponential.

c)

$$\begin{aligned} i &= \frac{1}{2}\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 \\ i &= \frac{1}{2}(400 \times 10^{-6}) \frac{0.72 \times 10^{-6}}{0.18 \times 10^{-6}} (0.7 - 0.5)^2 \\ i &= 32 \mu\text{A} \end{aligned}$$

$$\begin{aligned} R &= \frac{V_{DD} - V_D}{i} \\ R &= \frac{1.8 - 0.7}{32 \times 10^{-6}} \\ R &= \boxed{34.375 \text{ k}\Omega} \end{aligned}$$

d)

$$i_{D2} = \frac{1}{2}\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$i_{D2} = \frac{1}{2}(400 \times 10^{-6}) \frac{2.16 \times 10^{-6}}{0.18 \times 10^{-6}} (0.7 - 0.5)^2$$
$$i_{D2} = \boxed{96 \mu\text{A}}$$

It doesn't matter what the value of R_2 is because the R_2 only sets $V_{D2} = V_{DD} - i_{D2}R_2$. The current is still determined by V_D and V_T .

e) Edge of saturation happens at pinchoff,

$$V_{D2} = V_{GS} - V_T$$
$$V_{D2} = 0.7 - 0.5$$
$$V_{D2} = 0.2 \text{ V}$$

$$R_2 = \frac{V_{DD} - V_{D2}}{i_{D2}}$$
$$R_2 = \frac{1.8 - 0.2}{96 \times 10^{-6}}$$
$$R_2 = \boxed{16.667 \text{ k}\Omega}$$

To be more in saturation, we want $V_{D2} > V_{GS} - V_T$. This will increase the 0.2 V term, decreasing R_2 . That means we want a smaller value of R_2 .

Problem 7.3. MIS Capacitors

An MIS capacitor is composed of an SiO_2 (relative permittivity = 3.9) dielectric of thickness 40 nm on top of p-type silicon with doping level $N_A = 10 \times 10^{17} \text{ cm}^{-3}$. Assume the threshold voltage is 0.5 V and a voltage of 1.8 V is applied to the capacitor.

- a) Calculate the induced surface charge density (charge per unit area) in the metal electrode. Are these charges positive or negative, mobile or stationary?
- b) What must the induced charge density be at the semiconductor surface?
- c) How much of the induced charge density at the semiconductor surface is due to stationary charges vs mobile charges?

Solution.

□

a)

$$\begin{aligned}\frac{Q}{A} &= \frac{\epsilon}{d} V \\ \frac{Q}{A} &= \frac{(3.9)(8.824 \times 10^{-12})}{40 \times 10^{-9}} (1.8) \times \frac{1 \text{ m}^2}{10\,000 \text{ cm}^2} \\ \frac{Q}{A} &= \boxed{1.549 \times 10^{-7} \text{ C/cm}^2}\end{aligned}$$

Positive mobile charges.

b)

$$\frac{Q}{A} = \boxed{-1.549 \times 10^{-7} \text{ C/cm}^2}$$

c) Almost all of the induced charge density at the surface is due to stationary charges because of inversion.

Problem 7.4. An MOSFET

A MOSFET is made with a dielectric composed of SiO_2 (relative permittivity = 3.9) and thickness 40 nm. The channel length is 180 nm and the channel width is 3 μm . The applied gate voltage is 3 V, the source voltage is 0 V, and the drain voltage is 0.5 V. The threshold voltage is 0.5 V. Assume the mobility of electrons to be $1000 \text{ cm}^2/\text{Vs}$.

- a) Calculate the drain current
- b) Calculate the equivalent resistance of the MOSFET assuming that its drain current rises linearly with its voltage up to the operating point in the problem.
- c) All else equal, if the drain voltage is gradually increased, at what value of drain voltage will the drain current saturate to a constant value? What will that constant value be?

Solution.

□

a)

$$i_D = \mu_n C_{ox} \frac{W}{L} [(V_{GS} - V_T)V_{DS} - V_{DS}^2/2]$$

$$i_D = (1000 \times 10^{-4}) \frac{(3.9)(8.854 \times 10^{-12})}{40 \times 10^{-9}} \frac{3 \times 10^{-6}}{180 \times 10^{-9}} [(3 - 0.5)(0.5) - (0.5)^2/2]$$

$$i_D = \boxed{1.619 \text{ mA}}$$

b)

$$R_{eq} = \frac{V_D}{i_D}$$

$$R_{eq} = \frac{0.5}{1.619 \times 10^{-3}}$$

$$R_{eq} = \boxed{308.833 \Omega}$$

c)

$$V_{DS} = V_{GS} - V_T$$

$$V_{DS} = 3 - 0.5$$

$$V_{DS} = \boxed{2.5 \text{ V}}$$

$$I_{D,\text{sat}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{DS}^2$$

$$I_{D,\text{sat}} = \frac{1}{2} (1000 \times 10^{-4}) \frac{(3.9)(8.854 \times 10^{-12})}{40 \times 10^{-9}} \frac{3 \times 10^{-6}}{180 \times 10^{-9}} (2.5)^2$$

$$I_{D,\text{sat}} = \boxed{4.496 \text{ mA}}$$

Problem 7.5. Small Signal Modeling

Consider the so-called “common-gate” amplifier below. For all parts, assume the following:


$$\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$$

$$\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$$

$$V_T = 0.4 \text{ V} \quad \text{for NMOS devices}$$

$$V_T = -0.4 \text{ V} \quad \text{for PMOS devices}$$

$$W/L = 10$$

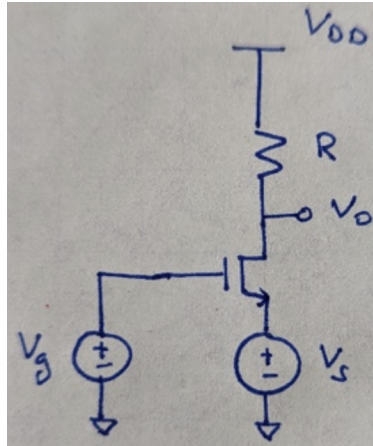

- An amplifier is made with an NMOS transistor as shown in the figure. $R = 2 \text{ k}\Omega$ and $V_{DD} = 2 \text{ V}$. The DC value of the gate voltage (V_G) is 0 V . Calculate the value of the input, V_S , that will result in the FET being at the edge of saturation.
- Calculate the small signal transconductance g_m for the MOSFET in (a).
- $v_S(t)$ has a dc value V_S calculated in (a) as well as small perturbation such that $v_S(t) = V_S + \tilde{v}_S$. Draw the small signal model of the amplifier and calculate the small signal voltage gain \tilde{v}_O/\tilde{v}_S . Let your answer be symbolic, i.e., a function of g_m and R rather than a number.
- At the output port, calculate the Thevenin equivalent of the small-signal model of the circuit as a function of g_m and R .
- At the input port (i.e., across v_S), calculate the Thevenin input impedance of the small signal model of the circuit as a function of g_m and R , assuming that the output is open circuited.

Solution.

□

a)

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_G - V_S - V_T)^2$$

$$i_D = \frac{1}{2} (200 \times 10^{-6}) (10) (0 - V_S - 0.4)^2$$

$$i_D = 10^{-3} (-V_S - 0.4)^2$$

$$V_{DS} = V_{GS} - V_T$$

$$V_D - V_S = V_G - V_S - V_T$$

$$V_D = V_G - V_T$$

$$V_{DD} - i_D R = V_G - V_T$$

$$2 - 10^{-3} (-V_S - 0.4)^2 (2000) = 0 - 0.4$$

$$2 - 2 (-V_S - 0.4)^2 = -0.4$$

$$2 - 2V_S^2 - 1.6V_S - 0.32 = -0.4$$

$$-2V_S^2 - 1.6V_S + 2.08 = 0$$

$$2V_S^2 + 1.6V_S - 2.08 = 0$$

$$V_S = \frac{-1.6 \pm \sqrt{1.6^2 - 4(2)(-2.08)}}{2(2)}$$

$$V_S = 0.695 \text{ V}$$

$$V_S = -1.495 \text{ V}$$

Test both solutions for inversion,

$$V_{GS} \geq V_T$$

$$V_G - V_S \geq V_T$$

$$0 - V_S \geq V_T$$

$$V_S \leq -V_T$$

$$0.695 \not\leq -0.4$$


$$-1.495 \leq -0.4$$

$$\boxed{V_S = -1.495 \text{ V}}$$

b)

$$\begin{aligned}
 i_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 \\
 g_m &= \frac{di_D}{dV_{GS}} = \frac{d}{dV_{GS}} \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 \\
 g_m &= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T) \\
 g_m &= \mu_n C_{ox} \frac{W}{L} (V_G - V_S - V_T) \\
 g_m &= (200 \times 10^{-6})(10)(0 - (-1.495) - 0.4) \\
 g_m &= \boxed{2.190 \text{ mS}}
 \end{aligned}$$

c) Small signal circuit,

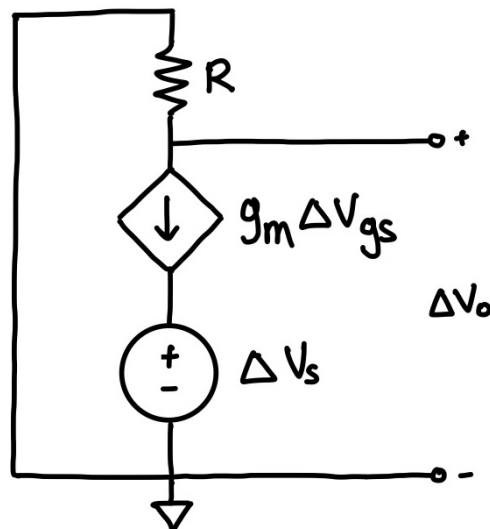

$$\begin{aligned}
 i &= g_m \Delta v_{gs} \\
 i &= g_m (0 - \Delta v_s) \\
 \Delta v_s &= -\frac{i}{g_m}
 \end{aligned}$$

$$\Delta v_o = -iR$$

$$\boxed{\frac{\Delta v_o}{\Delta v_s} = g_m R}$$

d)

$$\frac{\Delta v_o}{\Delta v_s} = g_m R$$

$$\Delta v_o = \boxed{V_{th} = g_m R \Delta v_s}$$

$$\boxed{R_{th} = R}$$

e)

$$\Delta i_s = g_m \Delta v_s$$

$$\frac{\Delta v_s}{\Delta i_s} = \frac{\Delta v_s}{g_m \Delta v_s}$$

$$\frac{\Delta v_s}{\Delta i_s} = \boxed{\frac{1}{g_m}}$$