

Q1 Solutions

a)

NMOS:

$$V_g = 0.4V$$

$$V_s = 0V$$

$$V_{gs} = 0.4V$$

$$V_t = 0.1V$$

$$I_n = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{gs} - V_t)^2 = 40 \mu A$$

PMOS:

$$V_g = 0.4$$

$$V_s = V_{dd} = 2V$$

$$V_{gs} = -1.6V$$

$$V_t = -0.3V$$

$$I_p = \mu_p C_{ox} \frac{W}{L} * \left((|V_{gs}| - |V_t|)^2 * |V_{ds}| - \frac{1}{2} V_{ds}^2 \right) = I_n = 40 \mu A$$

$$V_{ds} = -0.00237V$$

$$V_{out} = 1.99763V \approx 2V$$

b)

i

$$V_{gs} = -2V,$$

$$V_t = 0.1V$$

$|V_{gs}| > |V_t|$, on

ii

$$V_{gs} = 0V$$

$$V_t = 0.1V$$

$V_{gs} < V_t$, off

iii

| Va | Vb | Vout |
|----|----|------|
| 0 | 0 | 1 |
| 1 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 1 | 0 |

NOR gate

Q2 solutions

a. $z_1 = \frac{2x^2 - y^2}{4x^2 + y^2} + \frac{3xy}{4x^2 + y^2}j$


$$z_2 = 3 \cos \theta - j \sin \theta$$

$$z_3 = -(\sin \theta + 2 \cos \theta) + j(\cos \theta - 2 \sin \theta)$$


$$z_4 = \cos \frac{n\pi}{4} - j \sin \frac{n\pi}{4}$$

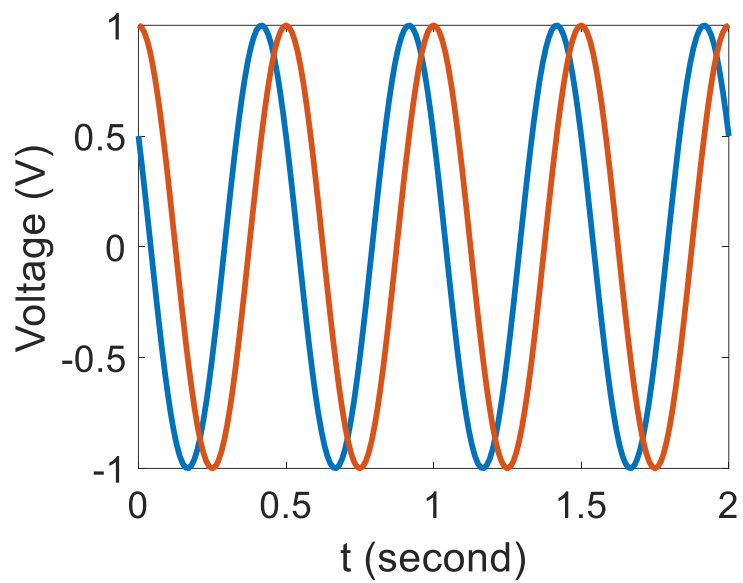b. $V = \cos\left(4\pi t + \frac{\pi}{3}\right)$, Amplitude: 1 V, Frequency: 2 Hz, Phase $\frac{\pi}{3}$

The new voltage signal $V' = \cos(4\pi t)$



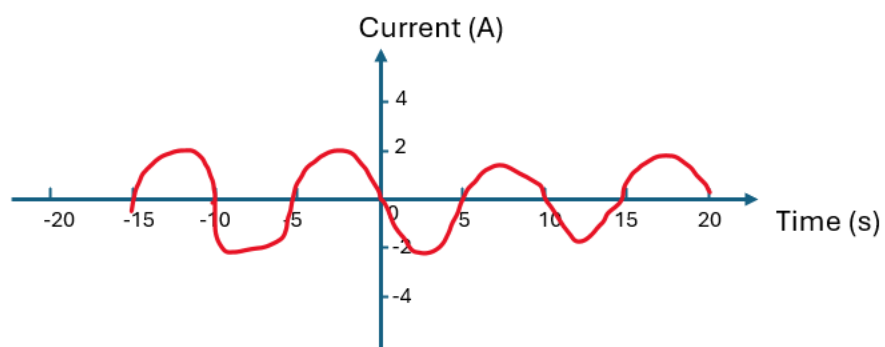c. $I = 2 \cos\left(0.2\pi t + \frac{\pi}{2}\right)$



Q3 (25 points)


(a) $Z_R = R = 1 \Omega$

$Z_L = j\omega L = j(2\pi \times 10^3 \times 10 \times 10^{-6}) = j0.002\pi = j6.28 \times 10^{-3} \Omega$

(b) $Z_R = R = 1 \Omega$

$Z_L = j\omega L = j(2\pi \times 10^6 \times 10 \times 10^{-6}) = j20\pi = j62.8 \Omega$

(c)

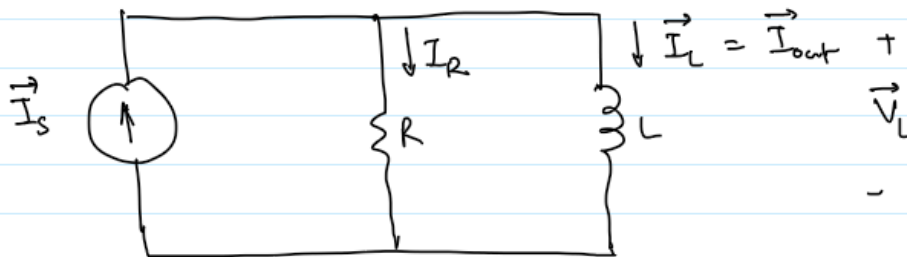

$$\frac{\vec{V}_R}{R} + \frac{\vec{V}_L}{j\omega L} - \vec{I}_s = 0 \Rightarrow \vec{V}_L \left(\frac{j\omega L + R}{j\omega L R} \right) = \vec{I}_s$$

$$\Rightarrow \vec{V}_L = \frac{j\omega L R}{R + j\omega L} \vec{I}_s$$

$$\vec{I}_L = \frac{\vec{V}_L}{j\omega L} = \vec{I}_s \frac{j\omega L R}{R + j\omega L} \cdot \frac{1}{j\omega L}$$

$$= \vec{I}_s \frac{R}{R + j\omega L}$$

$$= \vec{I}_s \frac{1}{1 + j\omega \frac{L}{R}}$$

$$\frac{\vec{I}_L}{\vec{I}_s} = \frac{1}{1 + j\omega \frac{L}{R}} = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} e^{-j \tan^{-1}\left(\frac{\omega L}{R}\right)}$$

(d) corner frequency $\omega_c = \frac{R}{L} = 10^5 \text{ rad/s}$

$$f_c = \frac{\omega_c}{2\pi} = 15.9 \text{ kHz}$$

Low-pass filter since low frequency signals are passed and high frequency signals are suppressed.

(f) At $f = 1 \text{ MHz}$, $\omega = 2\pi f = 2 \times 10^6 \pi = 6.28 \times 10^6 \text{ rad/s}$

$$\left| \frac{I_L}{I_s} \right| = \frac{1}{\sqrt{1 + \left(\frac{6.28 \times 10^6}{10^5} \right)^2}} = 0.0159$$


$$\angle \left(\frac{I_L}{I_s} \right) = -\tan^{-1} \left(\frac{6.28 \times 10^6}{10^5} \right) = -1.55 \text{ rad} = -89.1^\circ$$

(g) From part (f), at $f = 1 \text{ MHz}$, $\left| \frac{I_L}{I_s} \right| = 0.0159$, $\angle \left(\frac{I_L}{I_s} \right) = -89.1^\circ$

magnitude of $I_L(t) = 2 \times 0.0159 = 0.0318 \text{ mA}$
phase of $I_L(t) = 60^\circ - 89.1^\circ = -29.1^\circ$
 $\approx -30^\circ$

$$\begin{aligned} \therefore I_L(t) &= 0.0318 \cos(2\pi 10^6 t - 29.1^\circ) \text{ mA} \\ &= 0.0318 \cos(6.28 \times 10^6 t - 29.1^\circ) \text{ mA} \\ &= 0.0318 \cos(6.28 \times 10^6 t - 0.508) \text{ mA} \end{aligned}$$

Q4

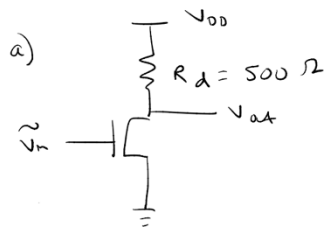

$$g_m = \frac{2I_D}{(V_{GS} - V_T)} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$$

$$I_D = 5 \text{ mA} = 5 \cdot 10^{-3} \text{ A}$$

$$V_{GS} = (2.5 \text{ V} - 0) = 2.5 \text{ V}$$

$$V_T = 2 \text{ V}$$

$$\Rightarrow V_{GS} - V_T = 0.5 \text{ V}$$

$$\Rightarrow \boxed{g_m = \frac{2(5 \cdot 10^{-3})}{0.5} = 0.02 \frac{\text{A}}{\text{V}}}$$

b) Constant voltage gain: can use the small signal model,

$$\frac{V_{out}}{V_{GS}} = -g_m R_L' \quad g_m = 0.02 \frac{\text{A}}{\text{V}}$$

$$R_L' = \frac{R_d R_L}{R_d + R_L} = \frac{(500)(2000)}{800} = 1250 \Omega$$

$$\Rightarrow \frac{V_{out}}{V_{GS}} = -(0.02)(1250) = \boxed{-25}$$

gain is 25, inverting


c)

$$\# \text{ dB} = 20 \log(\#)$$

$$= 20 \log(8)$$

$$= 20(0.9031)$$
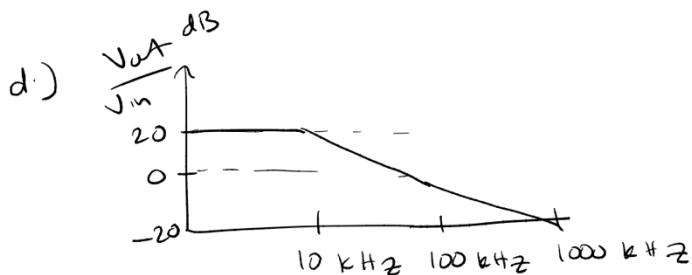
$$\boxed{\# \text{ dB} = 18.06} \approx 20 \text{ dB.}$$



Low pass filter since lower frequencies see high gain, higher frequencies are suppressed.

e) Rolls off at -20 dB/decade .

So at $1 \text{ MHz} (= 1000 \text{ kHz})$


at $\boxed{-20 \text{ dB}}$

$$-20 \text{ dB} = 20 \log(x)$$

$$-1 = \log(x)$$

$$10^{-1} = x \Rightarrow \boxed{\text{gain is } \frac{1}{10}}$$

f)

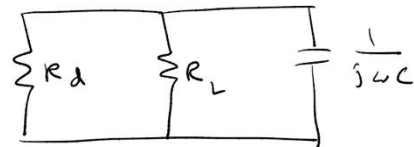

$$\boxed{\frac{1}{Z_{\text{total}}} = \frac{1}{R_d} + \frac{1}{R_L} + j\omega C}$$