

Introduction to Electrical Engineering (ECE 302H) – Homework 1

Dawson Zhang | Instructor: Dr. Hanson

Fall 2025

1 Problems

Problem 1.1. LTSpice Tutorial



Remark. Not copying in the entire problem statement... refer to the HW sheet


Solution.

□

K) $V_{out} = 1.5 \text{ V}$, $V_{out2} = 1.5 \text{ V}$

I)

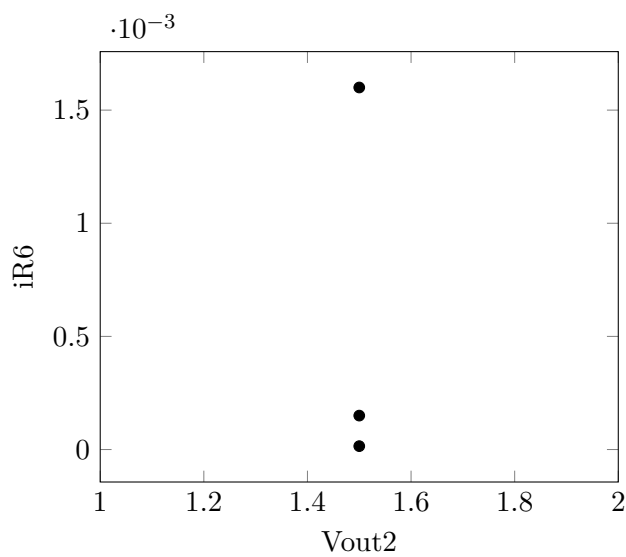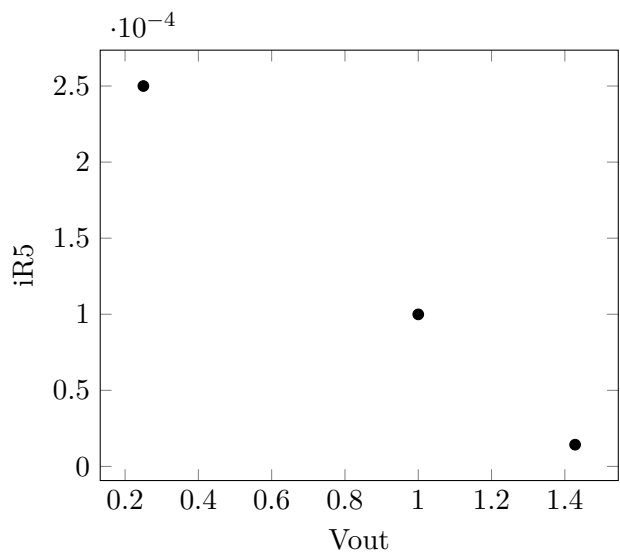

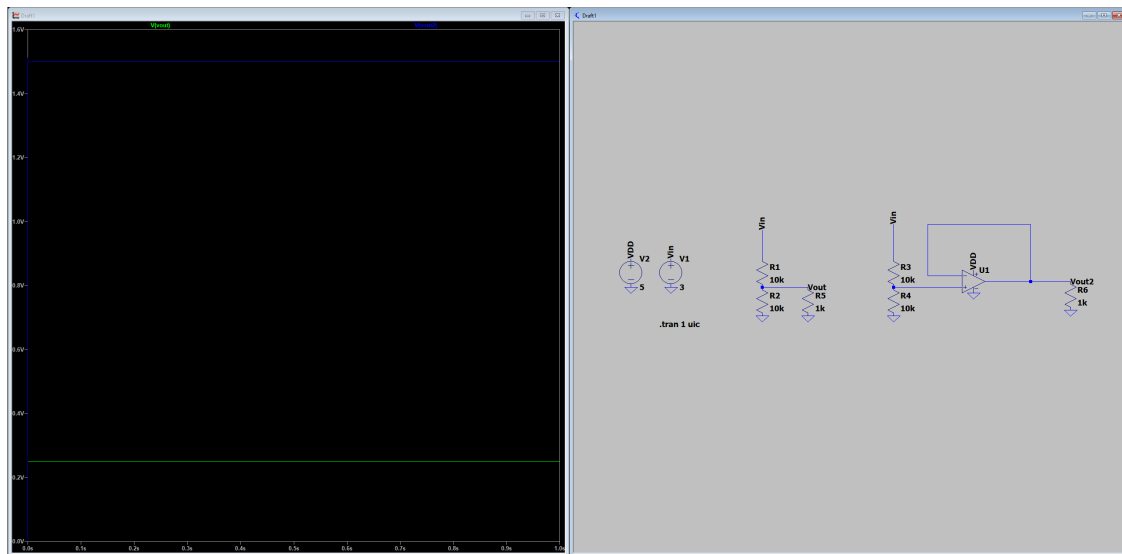

M) The main difference between the two circuits is that the second one always outputs a constant voltage. This is advantageous because there might be electrical components that require a certain voltage or may experience unintended behaviors when operating at lower or higher voltages.

Problem 1.2. System of Equations by Hand

1. Solve for x and y :

$$2x + 6y = 36$$

$$7x - 3y = 6$$

2. Solve for x , y , and z :

$$\frac{1}{8}x + \frac{1}{2}y - \frac{1}{4}z = -\frac{1}{2}$$

$$\frac{2}{3}x - \frac{1}{4}y + \frac{1}{6}z = \frac{7}{2}$$

$$\frac{1}{3}x + y - \frac{1}{3}z = \frac{2}{3}$$

3. Solve for x , y , and z in terms of a :

$$4x - 2y + 6z = 10 + 18a$$

$$6x + 4y - z = 22$$

$$2x + 8y - 5z = 14 - 16a$$

Solution.

□

1. Multiply the second equation by 2:

$$7x - 3y = 6$$

$$2(7x - 3y) = 2(6)$$

$$14x - 6y = 12$$

Add both equations:

$$\begin{cases} 2x + 6y = 36 \\ 14x - 6y = 12 \end{cases} \Rightarrow 16x = 48$$

$$\boxed{x = 3}$$

Substitute x back into first equation:

$$2x + 6y = 36$$

$$2(3) + 6y = 36$$

$$6y = 30$$

$$\boxed{y = 5}$$

2. Multiply the second equation by 2:

$$\begin{aligned}\frac{2}{3}x - \frac{1}{4}y + \frac{1}{6}z &= \frac{7}{2} \\ 2\left(\frac{2}{3}x - \frac{1}{4}y + \frac{1}{6}z\right) &= 2\left(\frac{7}{2}\right) \\ \frac{4}{3}x - \frac{1}{2}y + \frac{1}{3}z &= 7\end{aligned}$$

Add with the first equations together:

$$\begin{cases} \frac{1}{8}x + \frac{1}{2}y - \frac{1}{4}z = -\frac{1}{2} \\ \frac{4}{3}x - \frac{1}{2}y + \frac{1}{3}z = 7 \end{cases} \Rightarrow \frac{35}{24}x + \frac{1}{12}z = \frac{13}{2}$$

Multiply the first equation by -2:

$$\begin{aligned}\frac{1}{8}x + \frac{1}{2}y - \frac{1}{4}z &= -\frac{1}{2} \\ -2\left(\frac{1}{8}x + \frac{1}{2}y - \frac{1}{4}z\right) &= -2\left(-\frac{1}{2}\right) \\ -\frac{1}{4}x - y + \frac{1}{2}z &= 1\end{aligned}$$

Add with the third equation:

$$\begin{cases} -\frac{1}{4}x - y + \frac{1}{2}z = 1 \\ \frac{1}{3}x + y - \frac{1}{3}z = \frac{2}{3} \end{cases} \Rightarrow \frac{1}{12}x + \frac{1}{6}z = \frac{5}{3}$$

Remark. With these two new equations, we have converted the x and z parts of the problem to a 2 equation 2 unknown system.

Solve x - z system:

$$\begin{cases} -2\left(\frac{35}{24}x + \frac{1}{12}z\right) = -2\left(\frac{13}{2}\right) \\ \frac{1}{12}x + \frac{1}{6}z = \frac{5}{3} \end{cases} \Rightarrow -\frac{17}{6}x = -\frac{34}{3}$$

$$\boxed{x = 4}$$

$$\begin{aligned}\frac{1}{12}(4) + \frac{1}{6}z &= \frac{5}{3} \\ \frac{1}{3} + \frac{1}{6}z &= \frac{5}{3} \\ \frac{1}{6}z &= \frac{4}{3}\end{aligned}$$

$$\boxed{z = 8}$$

Plug x and z terms back into first equation:

$$\frac{1}{8}(4) + \frac{1}{2}y - \frac{1}{4}(8) = -\frac{1}{2}$$

$$\frac{1}{2}y = 1$$

$$\boxed{y = 2}$$

3. Eliminate y from first and second equations:

$$\begin{cases} 2(4x - 2y + 6z) = 2(10 + 18a) \\ 6x + 4y - z = 22 \end{cases} \Rightarrow 14x + 11z = 42 + 36a$$

Eliminate y from first and third equations:

$$\begin{cases} 4(4x - 2y + 6z) = 4(10 + 18a) \\ 2x + 8y - 5z = 14 - 16a \end{cases} \Rightarrow 18x + 19z = 54 + 56a$$

Solve for x and z :

$$\begin{cases} -\frac{9}{7}(14x + 11z) = -\frac{9}{7}(42 + 36a) \\ 18x + 19z = 54 + 56a \end{cases} \Rightarrow \frac{34}{7}z = \frac{68}{7}a$$

$$\boxed{z = 2a}$$

$$14x + 11(2a) = 42 + 36a$$

$$14x = 42 + 14a$$

$$\boxed{x = a + 3}$$

Solve for y using second equation:

$$6(a + 3) + 4y - (2a) = 22$$

$$4y = -4a + 4$$

$$\boxed{y = -a + 1}$$

Problem 1.3. Charge Carriers and Current

While current into and out of batteries is mediated by electrons, internally the flow of electricity is mediated by ions. Traditional batteries rely on a single species of ion (for example, Lithium ions Li^+) traveling between the cathode (+) and anode (-). Novel “dual-ion” batteries have two species of ion flowing simultaneously, such as batteries based on sodium hexafluorophosphate (NaPF_6). Imagine a battery oriented in the z direction with the cathode at the top (positive z) and the anode at the bottom (negative z). If 3×10^{20} hexafluorophosphate ions (PF_6^-) go through the interior of the battery in the positive z direction in 4 seconds, and simultaneously 1.5×10^{20} sodium ions (Na^+) go through the same cross section in the negative z direction, what is the magnitude and direction of the current flowing through the cross section? Is the battery being charged or discharged?

Solution. □

The magnitude of electrical current can be determined by calculating the net current through the battery. This first involves finding the current caused by each individual ion.

$$I = \frac{C}{s}$$

$$C = 6.24 \times 10^{18} e$$

Remark. Because the problem statement mentions the parallels between electrons and ions when talking about current in batteries, I’m making the assumption that the numerical number of ions can be used in place of electrons, and that the difference in electrons between hexafluorophosphate and sodium can be disregarded.

$$C_{\text{PF}_6^-} = \frac{3 \times 10^{20}}{6.24 \times 10^{18}} (-e) = -48.08$$

$$C_{\text{Na}^+} = \frac{1.5 \times 10^{20}}{6.24 \times 10^{18}} (+e) = 24.04$$

$$i_{\text{PF}_6^-} = \frac{-48.08}{4} = -12.02 \text{ A}_{+z} = 12.02 \text{ A}_{-z}$$

$$i_{\text{Na}^+} = \frac{24.04}{4} = 6.01 \text{ A}_{-z}$$

$$\sum I = 12.02 + 6.01 = \boxed{18.03 \text{ A}_{-z}}$$

Because the net current flows from cathode to anode, the battery is being charged.

Problem 1.4. Power and Energy

I would like to bake some cookies in my electric oven which operates at 120 V. During pre-heating, the oven operates at its rated power of 0.6 kW. However, after pre-heating, the oven only needs to consume 0.25 kW to maintain temperature. How much current does the oven draw in each case? How much energy does it consume during the 20-minute pre-heat and the 12-minute baking time? How many batches of cookies would I need to bake to use the same amount of energy in baking as I did in pre-heating?

Solution.

□

$$\begin{aligned}
 P &= IV \\
 I &= \frac{P}{V} \\
 I_{\text{pre-heat}} &= \frac{600}{120} = \boxed{5 \text{ A}} \\
 I_{\text{heated}} &= \frac{250}{120} = \boxed{2.08 \text{ A}}
 \end{aligned}$$

Remark. The approach I'm taking for this next step comes from knowing that potential is a joule per coulomb. If current is defined as a coulomb per second, we can find the amount of charge (coulombs) in both scenarios and add them because we have already found the amperage for each case.

$$\begin{aligned}
 I &= \frac{C}{s} \\
 C &= Is \\
 C_{\text{pre-heat}} &= (5)(20 \times 60) = 6000 \text{ C} \\
 C_{\text{heated}} &= (2.08)(12 \times 60) = 1500 \text{ C}
 \end{aligned}$$

$$\begin{aligned}
 V &= \frac{J}{C} \\
 J &= VC \\
 E_{\text{pre-heat}} &= (120)(6000) = \boxed{720 \text{ kJ}} \\
 E_{\text{heated}} &= (120)(1500) = \boxed{180 \text{ kJ}}
 \end{aligned}$$

To find the number of batches of cookies to bake to equal the amount of energy it took in pre-heating, assuming each batch of cookies takes 12-minutes to bake, we would just divide the pre-heating energy by the energy it took one batch to bake.

$$\text{Batches} = \frac{720}{180} = \boxed{4}$$

Problem 1.5. Passive Sign Convention

Before solving a problem, we usually label the voltage across and current through each component with variable names and reference directions. Four students labeled a component's voltage and current before solving a problem, each in a different way, as shown in the Figure (the Figure shows a resistor, but it could be any component). That actual polarity and magnitude of the voltage and current are also in the Figure. The students all solved the problem correctly. For each student, please answer the following:

1. How would the student write down their numerical answer for the voltage across and current through the resistor? In other words, what are i_a , v_a , i_b , and v_b ?
2. Does the student's labeling conform to the passive sign convention?
3. If the student calculated power as $v \times i$, what numerical answer would they get?
4. Would the student interpret their power number as power entering or leaving the resistor?

Finally, write a few sentences answering whether it is necessary to follow the passive sign convention when assigning reference directions, and what advantages or disadvantages it may provide to follow the convention.

Solution.

□

1. a)

$$i_a = 1 \text{ A} \quad v_a = 5 \text{ V}$$

- b) **Yes**

- c)

$$P = v \times i = 5 \text{ W}$$

- d) The student would interpret power as entering the resistor

2. a)

$$i_a = 1 \text{ A} \quad v_a = -5 \text{ V}$$

- b) **No**

- c)

$$P = v \times i = -5 \text{ W}$$

- d) The student would **still** interpret power as entering the resistor because in the end they all solved the problem correctly.

3. (a)

$$i_a = -1 \text{ A} \quad v_a = 5 \text{ V}$$

- (b) **No**

(c)

$$P = v \times i = \boxed{-5 \text{ W}}$$

(d) The student would **still** interpret power as entering the resistor because in the end they all solved the problem correctly.

4. (a)

$$\boxed{i_a = -1 \text{ A} \quad v_a = -5 \text{ V}}$$

(b) **Yes**

(c)

$$P = v \times i = \boxed{5 \text{ W}}$$

(d) The student would interpret power as entering the resistor

The passive sign convention is by no means necessary when assigning reference directions, however, utilizing it allows the numerical value of power to be directly interpreted. And, it also helps reduce the amount of negative-positive sign flipping.


Problem 1.6. Solving a Circuit

Remark. Not copying in the entire problem statement... refer to the HW sheet

Solution.

□

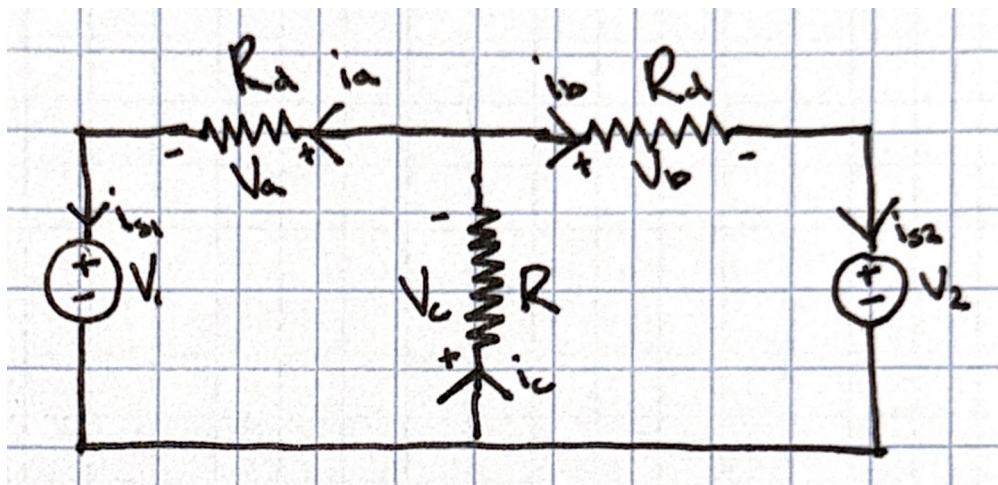- a) If different voltage DERs are connected together in the same grid, the path of least resistance would pass through both DERs and result in a short circuit, which could potentially set fire to the DERs.
- b) Refer to the following figure for correct labeling of the circuit:



Find KVL equations:

$$\sum V = V_1 + V_a + V_c = 0 \quad (1)$$

$$\sum V = V_2 + V_b + V_c = 0 \quad (2)$$

$$\sum V = V_1 + V_a - V_b - V_2 = 0 \quad (3)$$

Find KCL equations:

$$\sum I = I_a - I_{s1} = 0 \Rightarrow I_a = I_{s1} \quad (4)$$

$$\sum I = I_b - I_{s2} = 0 \Rightarrow I_b = I_{s2} \quad (5)$$

$$\sum I = I_c - I_a - I_b = 0 \quad (6)$$

$$\sum I = I_{s1} + I_{s2} - I_c = 0 \Rightarrow I_c = I_{s1} + I_{s2} \quad (7)$$

Find I-V relationships:

$$V_1 = V_1 \quad (\text{constant}) \quad (8)$$

$$V_2 = V_2 \quad (\text{constant}) \quad (9)$$

$$V_a = I_a R_d = I_{s1} R_d \quad (4) \quad (10)$$

$$V_b = I_b R_d = I_{s2} R_d \quad (5) \quad (11)$$

$$V_c = I_c R = (I_{s1} + I_{s2}) R \quad (7) \quad (12)$$

$$(13)$$

Substitute I-V relationships into KVL equations:

$$V_1 + V_a + V_c = 0 \quad (1)$$

$$V_1 + I_{s1} R_d + (I_{s1} + I_{s2}) R = 0 \quad (4)(7)$$

$$V_2 + V_b + V_c = 0 \quad (2)$$

$$V_2 + I_{s2} R_d + (I_{s1} + I_{s2}) R = 0 \quad (5)(7)$$

Remark. Notice now we have a 2-unknown 2-equation system of equations which we can solve for I_{s1} and I_{s2} .

$$\begin{cases} V_1 + I_{s1} R_d + (I_{s1} + I_{s2}) R = 0 \\ - V_2 + I_{s2} R_d + (I_{s1} + I_{s2}) R = 0 \end{cases} \Rightarrow V_1 + I_{s1} R_d - V_2 - I_{s2} R_d = 0$$

$$I_{s2} = \frac{V_1 + I_{s1} R_d - V_2}{R_d}$$

Substitute I_{s2} back in and solve for I_{s1} :

$$V_1 + I_{s1} R_d + (I_{s1} + \frac{V_1 + I_{s1} R_d - V_2}{R_d}) R = 0$$

$$V_1 + I_{s1} R_d + (\frac{V_1 + 2I_{s1} R_d - V_2}{R_d}) R = 0$$

$$V_1 + I_{s1} R_d + \frac{RV_1 + 2RI_{s1} R_d - RV_2}{R_d} = 0$$

$$V_1 + I_{s1} R_d + 2RI_{s1} + \frac{RV_1 - RV_2}{R_d} = 0$$

$$V_1 + \frac{RV_1 - RV_2}{R_d} = -I_{s1} R_d - 2RI_{s1}$$

$$\frac{V_1 R_d + RV_1 - RV_2}{R_d} = I_{s1} (-R_d - 2R)$$

$$\frac{V_1 R_d + RV_1 - RV_2}{R_d (-R_d - 2R)} = I_{s1}$$

$$\boxed{\frac{V_1 R_d + RV_1 - RV_2}{-R_d^2 - 2RR_d}} = I_{s1} = I_a \quad (4)$$

Substitute I_{s1} back in and solve for I_{s2} :

$$\begin{aligned}
 I_{s2} &= \frac{V_1 + I_{s1}R_d - V_2}{R_d} \\
 &= \frac{V_1 + \left(\frac{V_1R_d + RV_1 - RV_2}{-R_d^2 - 2RR_d} \right) R_d - V_2}{R_d} \\
 &= \frac{V_1}{R_d} + \frac{V_1R_d + RV_1 - RV_2}{-R_d^2 - 2RR_d} - \frac{V_2}{R_d} \\
 &= \frac{V_1(-R_d - 2R)}{R_d(-R_d - 2R)} + \frac{V_1R_d + RV_1 - RV_2}{-R_d^2 - 2RR_d} - \frac{V_2(-R_d - 2R)}{R_d(-R_d - 2R)} \\
 &= \frac{-V_1R_d - 2RV_1}{-R_d^2 - 2RR_d} + \frac{V_1R_d + RV_1 - RV_2}{-R_d^2 - 2RR_d} - \frac{-V_2R_d - 2RV_2}{-R_d^2 - 2RR_d} \\
 &= \boxed{\frac{V_2R_d + RV_2 - RV_1}{-R_d^2 - 2RR_d}} = I_b \quad (5)
 \end{aligned}$$

Calculate grid voltage V_c :

$$\begin{aligned}
 V_c &= (I_{s1} + I_{s2})R \quad (12) \\
 &= \left(\frac{V_1R_d + RV_1 - RV_2}{-R_d^2 - 2RR_d} + \frac{V_2R_d + RV_2 - RV_1}{-R_d^2 - 2RR_d} \right) R \\
 &= \left(\frac{V_1R_d + V_2R_d}{-R_d^2 - 2RR_d} \right) R \\
 &= \boxed{\left(\frac{V_1 + V_2}{-R_d - 2R} \right) R}
 \end{aligned}$$

Calculate ratio $\frac{I_a}{I_b}$:

$$\begin{aligned}
 \frac{I_a}{I_b} &= \frac{\frac{V_1R_d + RV_1 - RV_2}{-R_d^2 - 2RR_d}}{\frac{V_2R_d + RV_2 - RV_1}{-R_d^2 - 2RR_d}} \\
 \frac{I_a}{I_b} &= \boxed{\frac{V_1R_d + RV_1 - RV_2}{V_2R_d + RV_2 - RV_1}}
 \end{aligned}$$

c) Rewrite as functions of R_d :

$$\begin{aligned}
 \frac{I_a}{I_b}(R_d) &= \frac{V_1R_d + RV_1 - RV_2}{V_2R_d + RV_2 - RV_1} \\
 V_c(R_d) &= \left(\frac{V_1 + V_2}{-R_d - 2R} \right) R
 \end{aligned}$$


Substitute in new given numerical constants:

$$\frac{I_a}{I_b}(R_d) = \frac{V_1 R_d + R V_1 - R V_2}{V_2 R_d + R V_2 - R V_1} = \frac{(105)R_d + (10)(105) - (10)(115)}{(115)R_d + (10)(115) - (10)(105)} = \frac{105R_d - 100}{115R_d + 100}$$

$$V_c(R_d) = \left(\frac{V_1 + V_2}{-R_d - 2R} \right) R = \left(\frac{105 + 115}{-R_d - 2(10)} \right) (10) = \frac{2200}{-R_d - 20}$$

$$\frac{V_c(R_d)}{110} = \frac{20}{-R_d - 20}$$

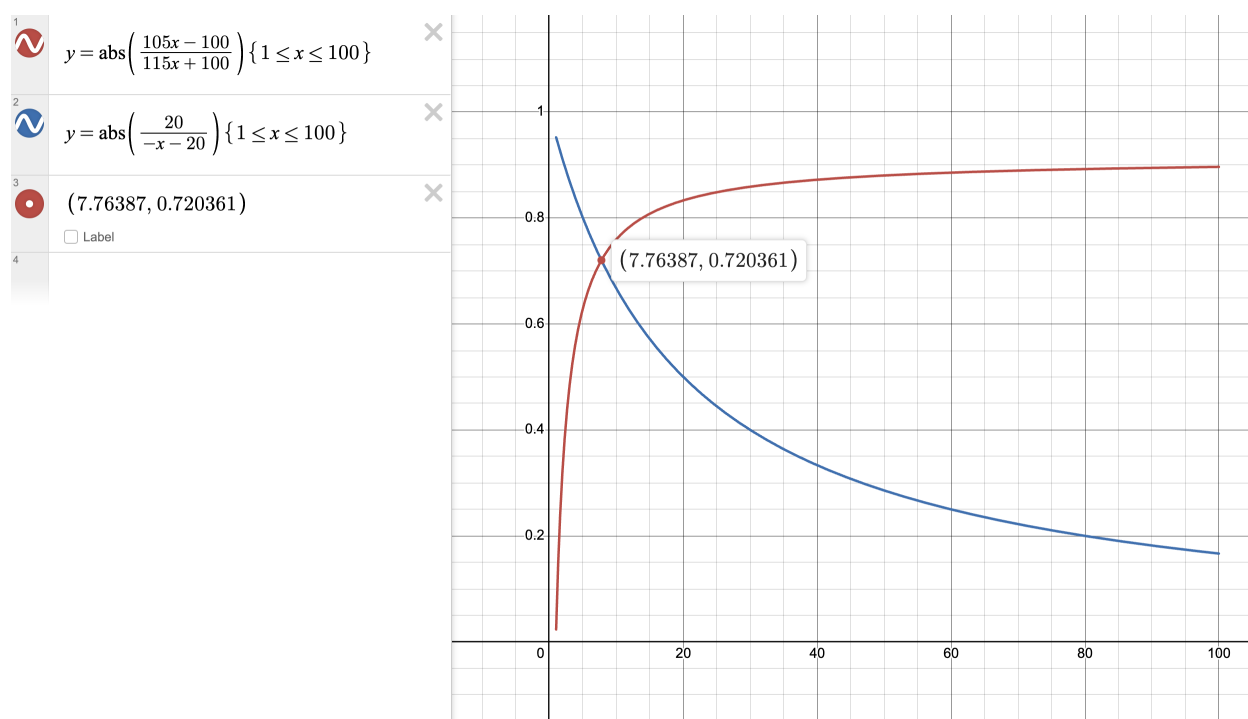Remark. When graphing these functions next, we only have to graph the magnitude of each function because the polarity of the current and voltage are known when given numerical constants.



- d) From the graph, we can see that when R_d gets too small there will be **high voltage** but a **greater difference** between the two currents, and when R_d gets too big there will be **low voltage** but a **smaller difference** between currents, which represents the trade off when choosing R_d .


Remark. It's important to note here that the red graph represents the ratio of of currents $\frac{I_a}{I_b}$ and not a numerical value for current, unlike the voltage graph. This means that as the ratio gets closer to 1, the numerical current values get closer to each other, and vice versa.

The way I like to think about this question is in terms of maximizing a function. It makes logical sense to set that function as some sort of a sum of $\left|\frac{I_a}{I_b}(R_d)\right|$ and $\left|\frac{V_c(R_d)}{110}\right|$.

$$f(R_d) = n \times \left|\frac{I_a}{I_b}(R_d)\right| + (1 - n) \times \left|\frac{V_c(R_d)}{110}\right|$$

where n is a coefficient from 0 to 1.

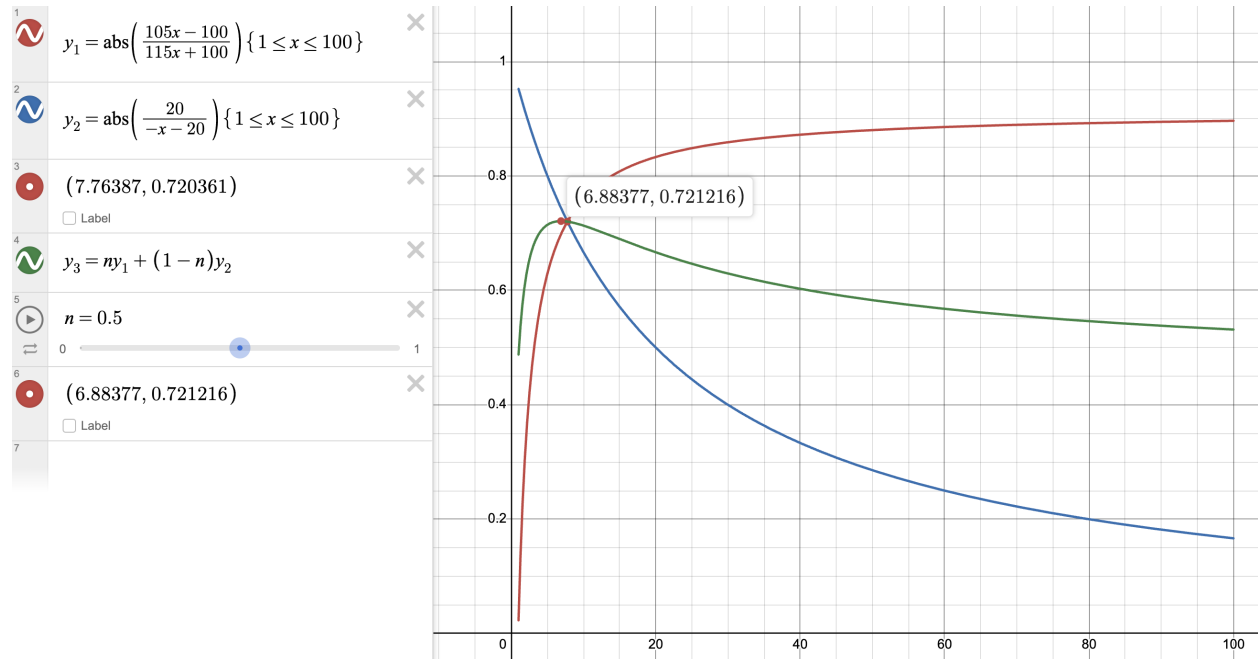If we set $n = 0.5$ that could be interpreted as an equal “weight” between voltage and current, and the resulting graph would look like:



The value of R_d that maximizes $f(R_d)$ when $n = 0.5$ is $R_d = 6.884$.

Remark. Depending on how you want to optimize between the ratio of voltage to current, a “good” value of R_d would change.