

Introduction to Electrical Engineering (ECE 302H) –

Homework 4

Dawson Zhang | Instructor: Dr. Hanson

Fall 2025

Problem 4.1. The most commonly-used nonlinear circuit component is the MOSFET. The I-V characteristic of the MOSFET (ignoring channel length modulation) is given by

$$i = \frac{1}{2}\mu_n C_{ox} \frac{W}{L} (v_{gs} - V_{TH})^2$$

- a) Formally show that this equation is nonlinear by using the definition of linearity.
- b) It is common for v_{gs} to be the sum of multiple sine waves. Let $v_{gs} = V_1 \sin(\omega t) + V_3 \sin(3\omega t)$, which can be modeled as two voltage sources in series, one of value $V_1 \sin(\omega t)$ and the other of value $V_3 \sin(3\omega t)$. With two sources, it may be tempting to apply superposition to the circuit to solve for the current, i.e. to solve for the current at 1ω and the current at 3ω separately. Show that this can not be done by calculating the current that you would get if you applied superposition and comparing it to the actual current. The fact that superposition does not work for nonlinear circuits will seriously hamper us later on. (You will learn later in the course that any periodic function can be represented by a sum of sine waves, one of the most impactful and remarkable observations of the 19th century)
- c) In HW3, we linearized the MOSFET (aka, we found the small-signal model for the MOSFET) by saying that each variable could be represented by an operating point plus a deviation. For example, $i \rightarrow I + \Delta i$. We then saw that the operating point terms on both sides cancelled and then we approximated any terms with a product of two deviations (e.g., Δv_{gs}^2) as zero. This time, linearize the equation above by taking the derivative of i with respect to v_{gs} and constructing a line that is tangent to the true $i(v_{gs})$ at an operating point (V_{gs}, I) .

Solution.

□

- a) Notice that there are a lot of constants in this equation that can be represented as a simple C variable for clarity.

Let,

$$C_1 = \frac{1}{2}\mu_n C_{ox} \frac{W}{L}$$

$$C_2 = V_{TH}$$

Rewrite the equation by substitution in C_1 and C_2 ,

$$i = \frac{1}{2}\mu_n C_{ox} \frac{W}{L} (v_{gs} - V_{TH})^2$$

$$i = C_1 (v_{gs} - C_2)^2$$

For the purposes of using the definition of linearity, I will represent $i(v_{gs})$ as $f(x)$. Rewrite the equation,

$$i(v_{gs}) = C_1(v_{gs} - C_2)^2$$

$$f(x) = C_1(x - C_2)^2$$

Recall that by the definition of linearity, the function f is linear if it satisfies,

$$f(au_1 + bu_2) = af(u_1) + bf(u_2)$$

Let $x = au_1 + bu_2$,

$$f(x) = C_1(x - C_2)^2$$

$$f(au_1 + bu_2) = C_1(au_1 + bu_2 - C_2)^2$$

Let $x = u_1$ and $x = u_2$,

$$f(x) = C_1(x - C_2)^2$$

$$f(u_1) = C_1(u_1 - C_2)^2$$

$$f(u_2) = C_1(u_2 - C_2)^2$$

Test linearity,

$$f(au_1 + bu_2) = C_1(au_1 + bu_2 - C_2)^2$$

$$af(u_1) + bf(u_2) = aC_1(u_1 - C_2)^2 + bC_1(u_2 - C_2)^2$$

Remark. You could distribute this out more to fully make sure that these aren't equal, but I think that it is pretty obvious these two equations can't possibly be equal. If you pay attention to the a and b , notice how in the first equation you will eventually get some a^2 and b^2 coefficient which is impossible to get in the second equation.

$$C_1(au_1 + bu_2 - C_2)^2 \neq aC_1(u_1 - C_2)^2 + bC_1(u_2 - C_2)^2$$

$$f(au_1 + bu_2) \neq af(u_1) + bf(u_2)$$

Not linear.

b) Apply the same constant substitution as in part a,

$$i = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{gs} - V_{TH})^2$$

$$i = C_1 (v_{gs} - C_2)^2$$

Consider the case when $v_{gs} = V_1 \sin(\omega t) + V_3 \sin(3\omega t)$,

$$i = C_1 (v_{gs} - C_2)^2$$

$$i = C_1 (V_1 \sin(\omega t) + V_3 \sin(3\omega t) - C_2)^2$$

This equation models the ACTUAL current that you would get without applying superposition.
Apply superposition $V_3 \sin(3\omega t) = 0$,

$$i = C_1 (v_{gs} - C_2)^2$$

$$i_1 = C_1 (V_1 \sin(\omega t) - C_2)^2$$

Apply superposition $V_1 \sin(\omega t) = 0$,

$$i = C_1 (v_{gs} - C_2)^2$$

$$i_2 = C_1 (V_3 \sin(3\omega t) - C_2)^2$$

Sum $i_1 + i_2$,

$$i = i_1 + i_2$$

$$i = C_1 (V_1 \sin(\omega t) - C_2)^2 + C_1 (V_3 \sin(3\omega t) - C_2)^2$$

Compare ACTUAL current and current calculated via superposition,

$$i_{\text{actual}} = C_1 (V_1 \sin(\omega t) + V_3 \sin(3\omega t) - C_2)^2$$

$$i_{\text{superposition}} = C_1 (V_1 \sin(\omega t) - C_2)^2 + C_1 (V_3 \sin(3\omega t) - C_2)^2$$

$$i_{\text{actual}} \neq i_{\text{superposition}}$$

Thus because the equation is not linear, we cannot apply superposition in this scenario.

c) Apply the same constant substitution as in part a and b,

$$i = \frac{1}{2}\mu_n C_{ox} \frac{W}{L} (v_{gs} - V_{TH})^2$$

$$i = C_1 (v_{gs} - C_2)^2$$

Take the derivative of $i(v_{gs})$,

$$i(v_{gs}) = C_1 (v_{gs} - C_2)^2$$

$$i'(v_{gs}) = 2C_1 (v_{gs} - C_2)$$

Slope of tangent line at V_{gs} ,

$$i'(v_{gs}) = 2C_1 (v_{gs} - C_2)$$

$$i'(V_{gs}) = 2C_1 (V_{gs} - C_2)$$

Equation for tangent line at (V_{gs}, I) ,

$$i - i_1 = i'(v_{gs_1})(v_{gs} - v_{gs_1})$$

$$i - I = 2C_1 (V_{gs} - C_2)(v_{gs} - V_{gs})$$


Substitute back in $C_1 = \frac{1}{2}\mu_n C_{ox} \frac{W}{L}$ and $C_2 = V_{TH}$,

$$i - I = 2C_1 (V_{gs} - C_2)(v_{gs} - V_{gs})$$

$$i - I = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{TH})(v_{gs} - V_{gs})$$

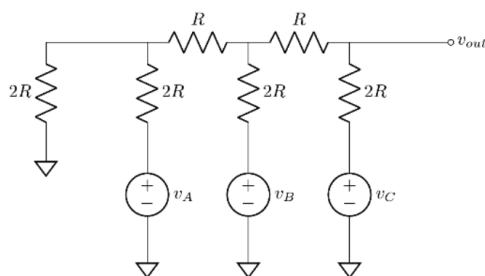Problem 4.2. Consider the circuit in the Figure composed of some resistors of value R and others with value $2R$.


- Use superposition to calculate the output voltage as a function of the inputs.
- Suppose that the inputs $V_a - V_c$ are digital values, i.e. they can only be equal to 0 or V_{DD} . This circuit is then a digital-to-analog converter (DAC). Explain how the DAC works in conceptual terms. How many different voltages can be produced in this DAC?
- Calculate the output if the digital input $[V_c \ V_b \ V_a] = [101]$.
- How would you create a similar DAC with twice as much resolution? (you do not need to show that it works; just draw the circuit)



Solution.

□

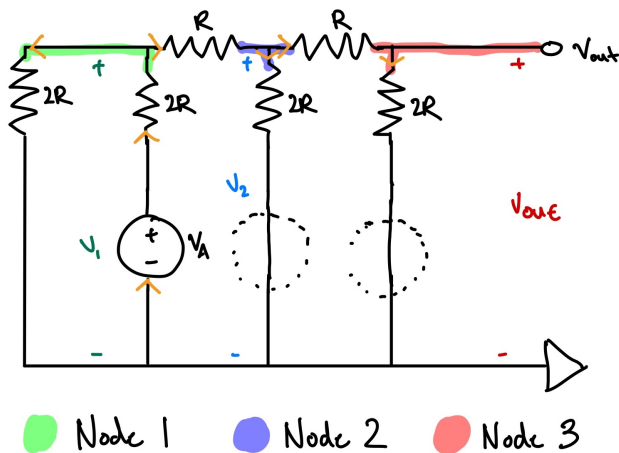- Superposition tells us that we need to solve for v_{out} by isolating each independent source. Begin by isolating v_A , AKA setting $v_B = 0$ and $v_C = 0$. Here's a redrawn circuit of what that will look like,



From here we can use node analysis to solve for v_{out} ,
KCLs:

$$\begin{aligned}\sum i &= \frac{v_A - v_1}{2R} - \frac{v_1 - 0}{2R} - \frac{v_1 - v_2}{R} = 0 \\ \sum i &= \frac{v_1 - v_2}{R} - \frac{v_2 - 0}{2R} - \frac{v_2 - v_{out}}{R} = 0 \\ \sum i &= \frac{v_2 - v_{out}}{R} - \frac{v_{out} - 0}{2R} = 0\end{aligned}$$

Rearrange first KCL:

$$\begin{aligned}\frac{v_A - v_1}{2R} - \frac{v_1 - 0}{2R} - \frac{v_1 - v_2}{R} &= 0 \\ v_A - v_1 - v_1 - 2v_1 + 2v_2 &= 0 \\ v_A + 2v_2 - 4v_1 &= 0 \\ 4v_1 &= v_A + 2v_2 \\ v_1 &= \frac{v_A + 2v_2}{4}\end{aligned}$$

Rearrange third KCL:

$$\begin{aligned}\frac{v_2 - v_{out}}{R} - \frac{v_{out} - 0}{2R} &= 0 \\ 2v_2 - 2v_{out} - v_{out} &= 0 \\ 2v_2 - 3v_{out} &= 0 \\ v_2 &= \frac{3}{2}v_{out}\end{aligned}$$

Substitute in v_2 into the first KCL:


$$\begin{aligned}v_1 &= \frac{v_A + 2v_2}{4} \\ v_1 &= \frac{v_A + 2\left(\frac{3}{2}v_{out}\right)}{4} \\ v_1 &= \frac{v_A + 3v_{out}}{4}\end{aligned}$$

Substitute v_1 and v_2 into second KCL:

$$\frac{v_1 - v_2}{R} - \frac{v_2 - 0}{2R} - \frac{v_2 - v_{out}}{R} = 0$$

$$\begin{aligned}
 2v_1 - 2v_2 - v_2 - 2v_2 + 2v_{out} &= 0 \\
 2v_{out} + 2v_1 - 5v_2 &= 0 \\
 2v_{out} + 2\left(\frac{v_A + 3v_{out}}{4}\right) - 5\left(\frac{3}{2}v_{out}\right) &= 0 \\
 2v_{out} + \frac{1}{2}v_A + \frac{3}{2}v_{out} - \frac{15}{2}v_{out} &= 0 \\
 \frac{1}{2}v_A &= 4v_{out} \\
 v'_{out} &= \frac{1}{8}v_A
 \end{aligned}$$

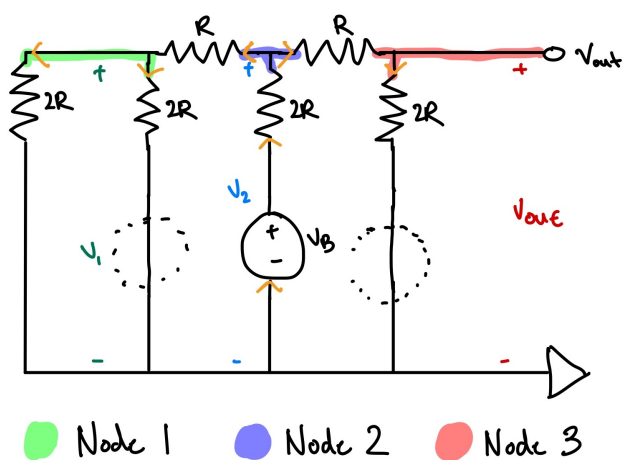Isolate v_B , ($v_A = v_C = 0$) and redraw,



KCLs:

$$\begin{aligned}
 \sum i &= \frac{v_2 - v_1}{R} - \frac{v_1 - 0}{2R} - \frac{v_1 - 0}{2R} = 0 \\
 \sum i &= \frac{v_B - v_2}{2R} - \frac{v_2 - v_1}{R} - \frac{v_2 - v_{out}}{R} = 0 \\
 \sum i &= \frac{v_2 - v_{out}}{R} - \frac{v_{out} - 0}{2R} = 0
 \end{aligned}$$

Rearrange first KCL:

$$\begin{aligned}
 \frac{v_2 - v_1}{R} - \frac{v_1 - 0}{2R} - \frac{v_1 - 0}{2R} &= 0 \\
 2v_2 - 2v_1 - v_1 - v_1 &= 0 \\
 2v_2 - 4v_1 &= 0 \\
 v_2 &= 2v_1
 \end{aligned}$$

Rearrange third KCL:

$$\begin{aligned}
 \frac{v_2 - v_{out}}{R} - \frac{v_{out} - 0}{2R} &= 0 \\
 2v_2 - 2v_{out} - v_{out} &= 0 \\
 2v_2 - 3v_{out} &= 0 \\
 v_2 &= \frac{3}{2}v_{out}
 \end{aligned}$$


Substitute in v_2 into the first KCL:

$$\begin{aligned}
 v_2 &= 2v_1 \\
 \frac{3}{2}v_{out} &= 2v_1 \\
 v_1 &= \frac{3}{4}v_{out}
 \end{aligned}$$

Substitute v_1 and v_2 into the second KCL:

$$\begin{aligned}
 \frac{v_B - v_2}{2R} - \frac{v_2 - v_1}{R} - \frac{v_2 - v_{out}}{R} &= 0 \\
 v_B - v_2 - 2v_2 + 2v_1 - 2v_2 + 2v_{out} &= 0 \\
 v_B + 2v_{out} + 2v_1 - 5v_2 &= 0 \\
 v_B + 2v_{out} + 2\left(\frac{3}{4}v_{out}\right) - 5\left(\frac{3}{2}v_{out}\right) &= 0 \\
 v_B + 2v_{out} + \frac{3}{2}v_{out} - \frac{15}{2}v_{out} &= 0 \\
 v_B &= 4v_{out} \\
 v_{out}'' &= \frac{1}{4}v_B
 \end{aligned}$$

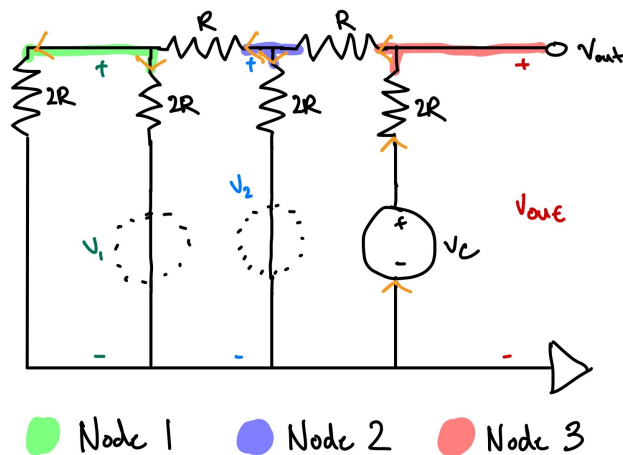Isolate v_C , ($v_A = v_B = 0$) and redraw,



KCLs:

$$\begin{aligned}\sum i &= \frac{v_2 - v_1}{R} - \frac{v_1 - 0}{2R} - \frac{v_1 - 0}{2R} = 0 \\ \sum i &= \frac{v_{out} - v_2}{R} - \frac{v_2 - v_1}{R} - \frac{v_2 - 0}{2R} = 0 \\ \sum i &= \frac{v_C - v_{out}}{2R} - \frac{v_{out} - v_2}{R} = 0\end{aligned}$$

Rearrange first KCL:

$$\begin{aligned}\frac{v_2 - v_1}{R} - \frac{v_1 - 0}{2R} - \frac{v_1 - 0}{2R} &= 0 \\ 2v_2 - 2v_1 - v_1 - v_1 &= 0 \\ 2v_2 - 4v_1 &= 0 \\ v_1 &= \frac{1}{2}v_2\end{aligned}$$

Substitute in v_1 into the second KCL:

$$\begin{aligned}\frac{v_{out} - v_2}{R} - \frac{v_2 - v_1}{R} - \frac{v_2 - 0}{2R} &= 0 \\ 2v_{out} - 2v_2 - 2v_2 + 2v_1 - v_2 &= 0 \\ 2v_{out} + 2v_1 - 5v_2 &= 0 \\ 2v_{out} + 2\left(\frac{1}{2}v_2\right) - 5v_2 &= 0 \\ 2v_{out} + v_2 - 5v_2 &= 0 \\ 2v_{out} - 4v_2 &= 0 \\ v_2 &= \frac{1}{2}v_{out}\end{aligned}$$

Substitute in v_2 into the third KCL:

$$\begin{aligned}\frac{v_C - v_{out}}{2R} - \frac{v_{out} - v_2}{R} &= 0 \\ v_C - v_{out} - 2v_{out} + 2v_2 &= 0 \\ v_C + 2v_2 - 3v_{out} &= 0 \\ v_C + 2\left(\frac{1}{2}v_{out}\right) - 3v_{out} &= 0 \\ v_C + v_{out} - 3v_{out} &= 0 \\ v_C - 2v_{out} &= 0 \\ v_{out} &= \frac{1}{2}v_C\end{aligned}$$

Sum together v_{out} superpositions,

$$v_{out} = v'_{out} + v''_{out} + v'''_{out}$$

$$v_{out} = \boxed{\frac{1}{8}v_A + \frac{1}{4}v_B + \frac{1}{2}v_C}$$

- b) The DAC works by taking digital inputs from $[v_A, v_B, v_C]$ and outputting an analog conversion of binary instruction since the coefficients of the inputs are consecutive multiples of 2 apart.

With this DAC, we can expect $\boxed{2^3 = 8}$ different voltage levels since we have three non identical inputs which can each be 0 or 1.

c)

$$v_A = v_C = V_{DD}$$


$$v_B = 0$$

$$v_{out} = \frac{1}{8}v_A + \frac{1}{4}v_B + \frac{1}{2}v_C$$

$$v_{out} = \frac{1}{8}v_{DD} + \frac{1}{4}(0) + \frac{1}{2}v_{DD}$$


$$v_{out} = \boxed{\frac{5}{8}v_{DD}}$$

- d) We could double the number of voltages by just adding a bit,

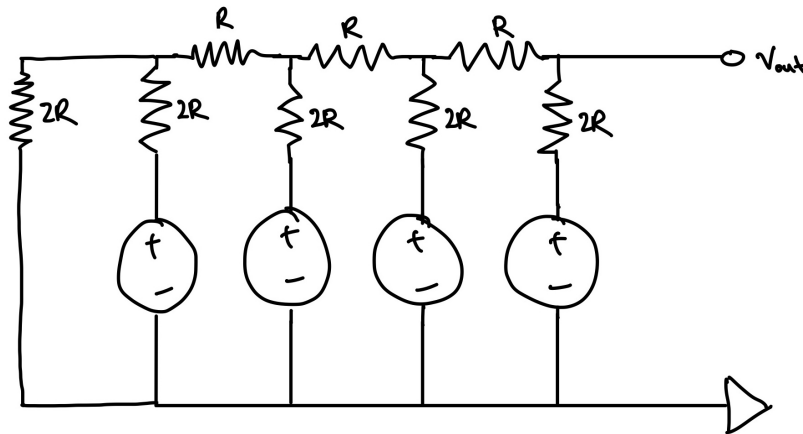

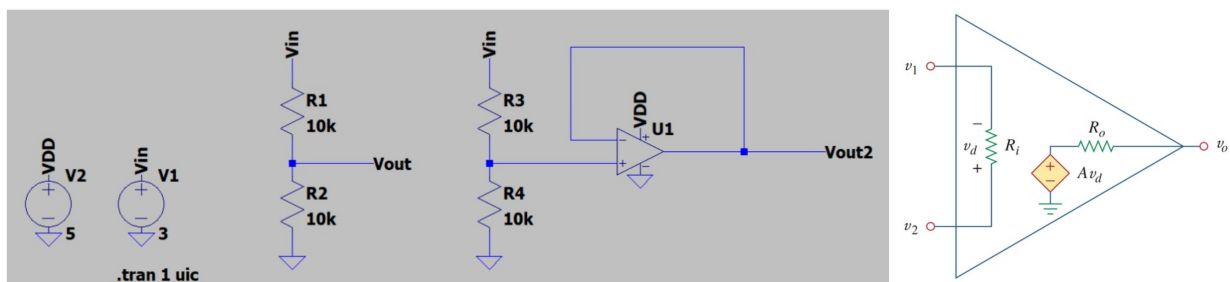Problem 4.3. Recall the two circuits that we simulated in HW1 and built in Lab 1: the resistive voltage divider, and the voltage divider plus op-amp, as recreated in the Figure.


- Find the Thevenin equivalent circuit for the voltage divider. Then, imagine that V_{out} is loaded with a current source of value i_{out} and plot V_{out} vs i_{out} using the Thevenin equivalent.
- Find the Thevenin equivalent circuit for the voltage divider plus op-amp circuit (the equivalent circuit model for the op-amp is given on the right; you may assume an ideal op-amp, namely $R_i = \infty$ and $R_o = 0$ and when you have the final answers, take the limit as $A \rightarrow \infty$). Then, imagine that V_{out2} is loaded with a current source of value i_{out} and plot V_{out} vs i_{out} using the Thevenin equivalent.
- Show that your results match what you found in HW1 and Lab 1.
- What advantage does the second circuit provide over the first circuit? State your answer in terms of Thevenin Equivalent Circuit parameters.



Solution.


□

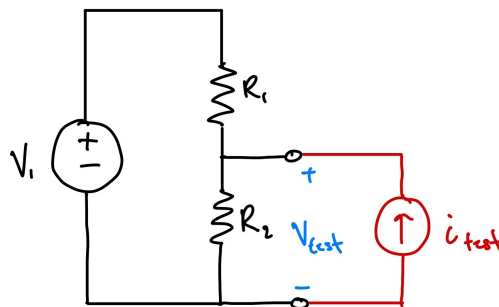- Apply test current source to voltage divider circuit,



Remark. In class we covered this problem by applying the superposition technique to solve for V_{test} so this will be mostly review.

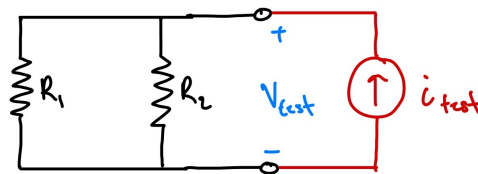Set up i_{test} superposition by setting $V_1 = 0$,




Calculate R_{eq} in parallel,

$$\begin{aligned}\frac{1}{R_{eq}} &= \frac{1}{R_1} + \frac{1}{R_2} \\ \frac{1}{R_{eq}} &= \frac{R_2}{R_1 R_2} + \frac{R_1}{R_1 R_2} \\ \frac{1}{R_{eq}} &= \frac{R_1 + R_2}{R_1 R_2} \\ R_{eq} &= \frac{R_1 R_2}{R_1 + R_2}\end{aligned}$$

Calculate voltage difference (V_{test}) through R_{eq} ,

$$\begin{aligned}V &= iR \\ V'_{test} &= \left(\frac{R_1 R_2}{R_1 + R_2} \right) i_{test}\end{aligned}$$

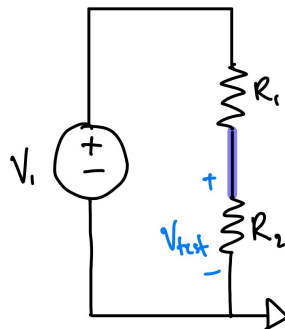Set up V_1 superposition by setting $i_{test} = 0$,



Perform clockwise current node analysis on highlighted node,

$$\begin{aligned}\sum i &= \frac{V_1 - V_{test}}{R_1} - \frac{V_{test} - 0}{R_2} = 0 \\ \frac{V_1}{R_1} - \frac{V_{test}}{R_1} - \frac{V_{test}}{R_2} &= 0 \\ \frac{V_1}{R_1} &= \frac{V_{test}}{R_1} + \frac{V_{test}}{R_2}\end{aligned}$$

$$\begin{aligned}\frac{V_1}{R_1} &= V_{test} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \\ \frac{V_1}{R_1} &= V_{test} \left(\frac{R_1 + R_2}{R_1 R_2} \right) \\ V_{test}' &= \frac{V_1}{R_1} \left(\frac{R_1 R_2}{R_1 + R_2} \right) \\ V_{test}'' &= \left(\frac{R_2}{R_1 + R_2} \right) V_1\end{aligned}$$


Combine superpositions,

$$\begin{aligned}V_{test} &= V_{test}' + V_{test}'' \\ V_{test} &= \left(\frac{R_2}{R_1 + R_2} \right) V_1 + \left(\frac{R_1 R_2}{R_1 + R_2} \right) i_{test}\end{aligned}$$


Thevenin equivalent,

$$\begin{aligned}V_{test} &= V_{th} + R_{th} i_{test} \\ V_{test} &= \frac{R_2 V_1}{R_1 + R_2} + \left(\frac{R_1 R_2}{R_1 + R_2} \right) i_{test}\end{aligned}$$

Plot V_{test} vs. i_{test} ,

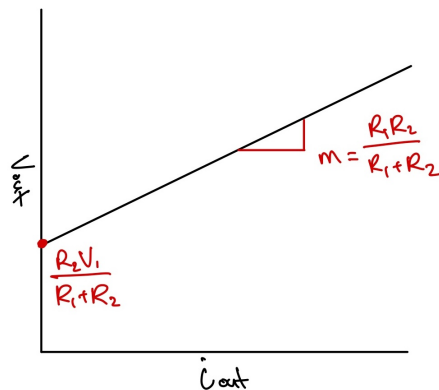

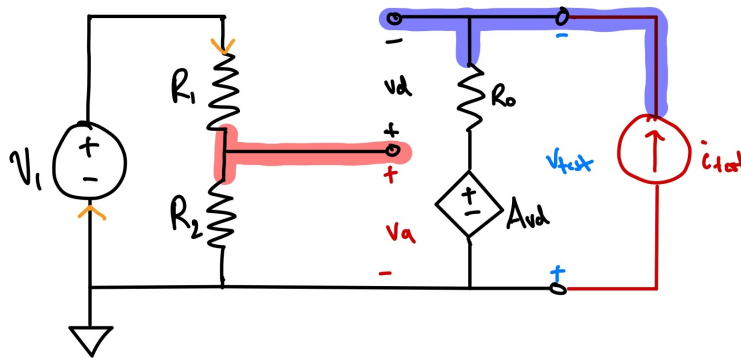- b) Redraw the circuit with the voltage divider plus equivalent op-amp circuit,



Perform node analysis to solve for v_{test} ,
KCLs,

$$\sum i = \frac{V_1 - V_a}{R_1} - \frac{V_a}{R_2} = 0$$

$$\sum i = i_{test} - \frac{V_{test} - AV_d}{R_0} = 0$$

Rearrange first equation,

$$\frac{V_1 - V_a}{R_1} - \frac{V_a}{R_2} = 0$$

$$\frac{V_1}{R_1} - \frac{V_a}{R_1} - \frac{V_a}{R_2} = 0$$

$$V_a \left(\frac{R_1 + R_2}{R_1 R_2} \right) = \frac{V_1}{R_1}$$

$$V_a = \left(\frac{R_2}{R_1 + R_2} \right) V_1$$

Rearrange second equation,

$$i_{test} - \frac{V_{test} - AV_d}{R_0} = 0$$

$$i_{test} - \frac{V_{test}}{R_0} + \frac{AV_d}{R_0} = 0$$

$$\frac{V_{test}}{R_0} = i_{test} + \frac{AV_d}{R_0}$$

$$V_{test} = R_0 i_{test} + AV_d$$

$$V_{test} = (0) i_{test} + AV_d$$

$$V_{test} = AV_d$$

From the the circuit,

$$\begin{aligned} V_a - V_d &= V_{test} \\ V_d &= V_a - V_{test} \\ V_d &= \left(\frac{R_2}{R_1 + R_2} \right) V_1 - V_{test} \end{aligned}$$


Plug back into second equation,

$$\begin{aligned} V_{test} &= AV_d \\ V_{test} &= A \left(\left(\frac{R_2}{R_1 + R_2} \right) V_1 - V_{test} \right) \\ \frac{V_{test}}{A} &= \left(\frac{R_2}{R_1 + R_2} \right) V_1 - V_{test} \\ \lim_{A \rightarrow \infty} \frac{V_{test}}{A} &= \lim_{A \rightarrow \infty} \left(\frac{R_2}{R_1 + R_2} \right) V_1 - V_{test} \\ 0 &= \left(\frac{R_2}{R_1 + R_2} \right) V_1 - V_{test} \\ V_{test} &= \left(\frac{R_2}{R_1 + R_2} \right) V_1 \end{aligned}$$

Thevenin equivalent,

$$\begin{aligned} V_{test} &= V_{th} + R_{th} i_{test} \\ V_{test} &= \boxed{\frac{R_2 V_1}{R_1 + R_2} + (0) i_{test}} \end{aligned}$$

Plot V_{test} vs. i_{test} ,

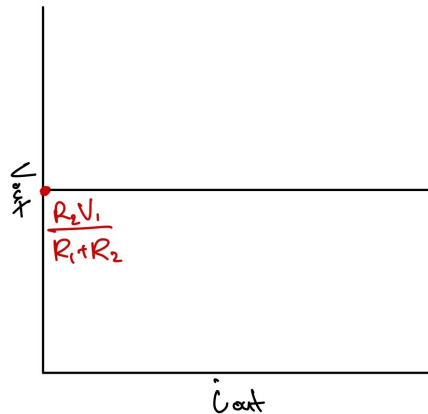

- c) Recall that Thevenin is in the form of

$$V_{test} = V_{th} + R_{th}i_{test}$$

In HW1 and Lab 1, we graphed the i-v relationship of the voltage divider and those results match what I found here. The voltage divider by itself yielded a linear i-v relationship which is consistent with what we found previously. The voltage divider plus op-amp circuit produces a constant i-v relationship which can be represented by a horizontal/vertical line and is also consistent with previous results.

- d) In the second circuit with ideal conditions $R_{th} \approx 0$, V_{test} barely changes with any load current. That means that it can maintain more load without affecting V_{test} . This relationship is reflected by the constant line on the i-v graph of the second circuit.

Problem 4.4. The Moku:Go has a signal generator that you want to use to excite a resistive circuit. The signal generator's Thevenin equivalent circuit is a voltage source with an output impedance of $200\ \Omega$.

- Use the concept of Thevenin/Norton equivalent circuits to explain why the resistive circuit can be modeled as a single resistor.
- You program the signal generator to output 5 V . What voltage will you see if the resistive circuit's equivalent resistance is the following? $R_{eq} \ll 200\ \Omega$, $R_{eq} \gg 200\ \Omega$, and $R_{eq} = 200\ \Omega$
- What resistive circuit equivalent resistance is required so that the actual voltage it experiences is within 1% of the voltage you programmed? Is that resistance a minimum or a maximum?
- A competing product, the Analog Discovery 2, has an output impedance of $20\ \Omega$. Is this better or worse than the Moku:Go? Explain your answer, including what you mean by "better."
- In Lab 1, you programmed the signal generator to produce 2 V but when we measured the output, it really produced 4 V . If you asked an experienced engineer what was happening, they might say "The signal generator's output resistance is $50\ \Omega$ and it's expecting to drive a matched load." Explain how this statement justifies why you saw 4 V in Lab 1 instead of 2 V .

Solution.

□

- For a purely resistive circuit without any independent sources, its Thevenin equivalent would just be equivalent to a resistance R_{eq} , and can be modeled by a single resistor.
-

$$V = \frac{R_{eq}}{R_s + R_{eq}} V_s$$

$$V = 5 \left(\frac{R_{eq}}{200 + R_{eq}} \right)$$

For the case $R_{eq} \ll 200\ \Omega$,

$$V \approx \lim_{R_{eq} \rightarrow 0} 5 \left(\frac{R_{eq}}{200 + R_{eq}} \right)$$

$$V \approx 5 \left(\frac{0}{200 + 0} \right)$$

$$V \approx \boxed{0\text{ V}}$$

For the case $R_{eq} \gg 200\ \Omega$,

$$\begin{aligned}
 V &\approx \lim_{R_{eq} \rightarrow \infty} 5 \left(\frac{R_{eq}}{200 + R_{eq}} \right) \\
 V &\approx \lim_{R_{eq} \rightarrow \infty} 5 \left(\frac{1}{\frac{200}{R_{eq}} + 1} \right) \\
 V &\approx 5 \left(\frac{1}{0 + 1} \right) \\
 V &\approx \boxed{5 \text{ V}}
 \end{aligned}$$

For the case $R_{eq} = 200 \Omega$,

$$\begin{aligned}
 V &= 5 \left(\frac{200}{200 + 200} \right) \\
 V &= 5 \left(\frac{1}{2} \right) \\
 V &= \boxed{2.5 \text{ V}}
 \end{aligned}$$

c)

$$\begin{aligned}
 V &= \frac{R_{eq}}{R_s + R_{eq}} V_s \\
 \frac{V}{V_s} &= \frac{R_{eq}}{R_s + R_{eq}} \geq 0.99
 \end{aligned}$$

Remark. We only care about 1% in the direction from 100% \rightarrow 99% and not from 100% \rightarrow 101% because the output voltage cannot physically be higher than the programmed voltage after passing through resistance.

$$\begin{aligned}
 \frac{R_{eq}}{R_s + R_{eq}} &\geq 0.99 \\
 R_{eq} &\geq 0.99(R_s + R_{eq}) \\
 R_{eq} &\geq 0.99R_s + 0.99R_{eq} \\
 R_{eq} - 0.99R_{eq} &\geq 0.99R_s \\
 R_{eq}(1 - 0.99) &\geq 0.99R_s \\
 R_{eq} &\geq \frac{0.99}{1 - 0.99} R_s \\
 R_{eq} &\geq 99R_s
 \end{aligned}$$

For $R_s = 200 \Omega$,

$$\begin{aligned}
 R_{eq} &\geq 99R_s \\
 R_{eq} &\geq 99(200) \\
 R_{eq} &\geq 19800 \\
 R_{eq} &\geq \boxed{19.8 \text{ k}\Omega}
 \end{aligned}$$

This is a minimum because $V \rightarrow V_s$ as $R_{eq} \rightarrow \infty$. This relationship was modeled in the previous part (b). $19.8 \text{ k}\Omega$ just represents the minimum resistance to remain within 1% of the programmed voltage when matched with an impedance of 200Ω .

- d) "Better" usually refers to less difference between the programmed voltage and actual voltage. In the case of the competing product with a lower R_s of 20Ω . The ratio

$$\frac{R_{eq}}{R_s + R_{eq}}$$

is closer to 1 than when $R_s = 200 \Omega$, so the competitor would be better.

Another way to think about this is that the competitor would “need” a lesser resistive circuit equivalent to be within the same difference of voltage.

For less than 1% difference,

$$\begin{aligned}
 R_{eq} &\geq 99(20) \\
 R_{eq} &\geq 1980 \\
 R_{eq} &\geq 1.98 \text{ k}\Omega
 \end{aligned}$$

$$1.98 \text{ k}\Omega < 19.8 \text{ k}\Omega$$

e)

$$\begin{aligned}
 V &= \frac{R_{eq}}{R_s + R_{eq}} V_s \\
 V &= \frac{50}{50 + 50} V_s \\
 V &= \frac{1}{2} V_s \\
 V_s &= 2V
 \end{aligned}$$

When $V = 2 \text{ V}$,

$$V_s = 2(2\text{ V})$$

$$V_s = 4\text{ V}$$

If the load is matched $R_{eq} = R_s$, then the ration between V_s and V would be 1:2. That's why we saw 4 V in Lab 1.

Problem 4.5. Suppose you have an unknown system (e.g., in a box). It is meant to take two voltages and one current as inputs v_1 , v_2 , i_3 and produce a single voltage as output v_o . All you know about the box is that the system inside is linear and the results of the following experiments, with voltages in volts and currents in amps.

	v_1	v_2	i_3	v_o
Experiment 1	3	2	1	37
Experiment 2	2	2	2	36
Experiment 3	1	5	3	44

Find the system equation, i.e. the equation that relates the inputs and the output. Be sure to include the units for each constant.

Solution.

□

Because the system is linear, we can model the equation with,

$$v_o = Av_1 + Bv_2 + Ci_3$$

where A and B have no units and C has units of ohms.

Convert the table into a system of three equations,

$$3A + 2B + C = 37$$

$$2A + 2B + 2C = 36$$

$$A + 5B + 3C = 44$$

$$\begin{cases} 3A + 2B + C = 37 \\ -2A - 2B - 2C = -36 \end{cases} \Rightarrow A - C = 1 \Rightarrow A = C + 1$$

$$3(C + 1) + 2B + C = 37$$

$$3C + 3 + 2B + C = 37$$

$$4C + 2B + 3 = 37$$

$$(C + 1) + 5B + 3C = 44$$

$$4C + 5B + 1 = 44$$

$$\begin{cases} 4C + 5B + 1 = 44 \\ -4C - 2B - 3 = 37 \end{cases} \Rightarrow 3B - 2 = 7 \Rightarrow B = 3$$

$$4C + 2(3) + 3 = 37$$

$$4C + 9 = 37$$

$$4C = 28$$

$$C = 7$$


$$A = C + 1$$

$$A = 7 + 1$$

$$A = 8$$

$$v_o = 8v_1 + 3v_2 + 7\Omega i_3$$

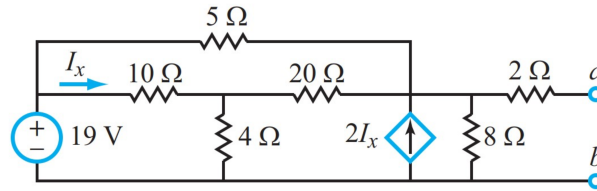
Problem 4.6. Find the Thevenin equivalent for the circuit below at the port consisting of terminals a and b. (Hint: as always, apply v_{test} and solve for i_{test} or apply i_{test} and solve for v_{test} . When solving, you may want/need to apply other techniques, such as node analysis or equivalent circuits.)



Solution.


□

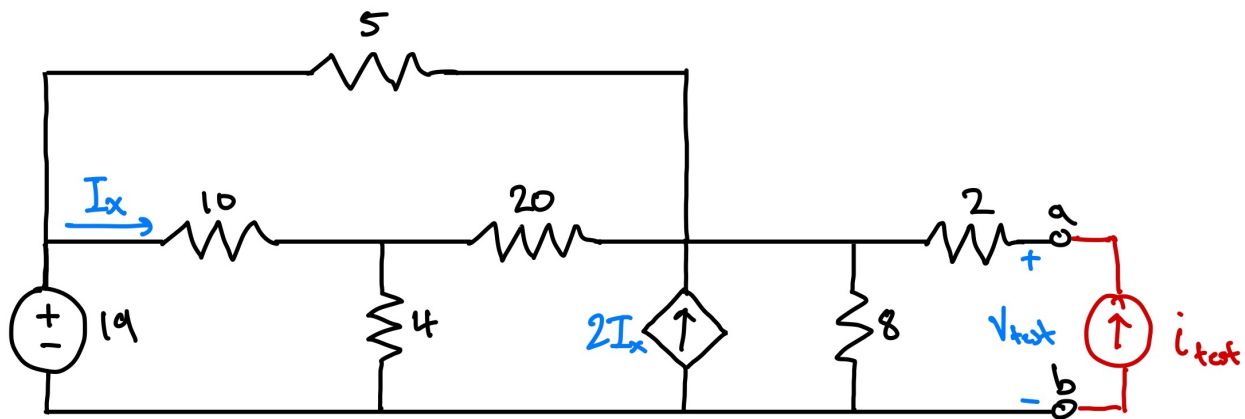Begin by drawing the circuit with a an i_{test} current source,



By performing superposition on both independent sources, we can solve for $v_{out} = v'_{out} + v''_{out}$

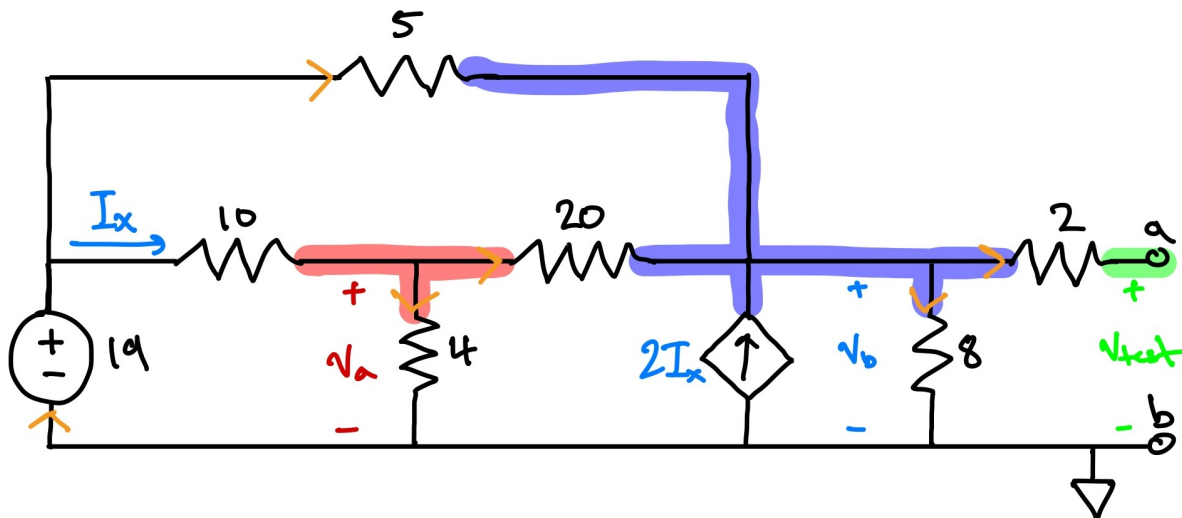Isolate the voltage source by setting $i_{test} = 0$,



KCLs,

$$\begin{aligned}\sum i &= \frac{19 - v_a}{10} - \frac{v_a - 0}{4} - \frac{v_a - v_b}{20} = 0 \\ \sum i &= 2I_x + \frac{v_a - v_b}{20} + \frac{19 - v_b}{5} - \frac{v_b - 0}{8} - \frac{v_b - v_{out}}{2} = 0 \\ \sum i &= \frac{v_b - v_{out}}{2} = 0\end{aligned}$$

i-v's,

$$I_x = \frac{19 - v_a}{10}$$

Solve for v'_{test} ,

$$\begin{aligned}\frac{v_b - v_{out}}{2} &= 0 \\ v_b - v_{out} &= 0 \\ v_b &= v_{out}\end{aligned}$$


$$\begin{aligned}\frac{v_b - v_a}{20} - \frac{v_a - 0}{4} - \frac{v_a - 0}{10} &= 0 \\ 38 - 2v_a - 5v_a - v_a + v_b &= 0 \\ 38 + v_b - 8v_a &= 0 \\ 38 + v_{test} - 8v_a &= 0 \\ v_a &= \frac{19}{4} + \frac{1}{8}v_{test}\end{aligned}$$

$$\begin{aligned}2I_x + \frac{v_a - v_b}{20} + \frac{19 - v_b}{5} - \frac{v_b - 0}{8} - \frac{v_b - v_{out}}{2} &= 0 \\ 40I_x + v_a - v_b + 76 - 4v_b - \frac{5}{2}v_b - 10v_b + 10v_{test} &= 0 \\ 76 - 4v_a + v_a - v_b + 76 - 4v_b - \frac{5}{2}v_b - 10v_b + 10v_{test} &= 0 \\ 76 - 4v_a + v_a - v_{test} + 76 - 4v_{test} - \frac{5}{2}v_{test} - 10v_{test} + 10v_{test} &= 0 \\ 152 - 3v_a - \frac{15}{2}v_{test} &= 0\end{aligned}$$

$$152 - 3v_a - \frac{15}{2}v_{test} = 0$$

$$\begin{aligned}
 152 - 3 \left(\frac{19}{4} + \frac{1}{8} v_{test} \right) - \frac{15}{2} v_{test} &= 0 \\
 152 - \frac{57}{4} - \frac{3}{8} v_{test} - \frac{15}{2} v_{test} &= 0 \\
 \frac{551}{4} - \frac{63}{8} v_{test} &= 0 \\
 v'_{test} &= \frac{1102}{63}
 \end{aligned}$$

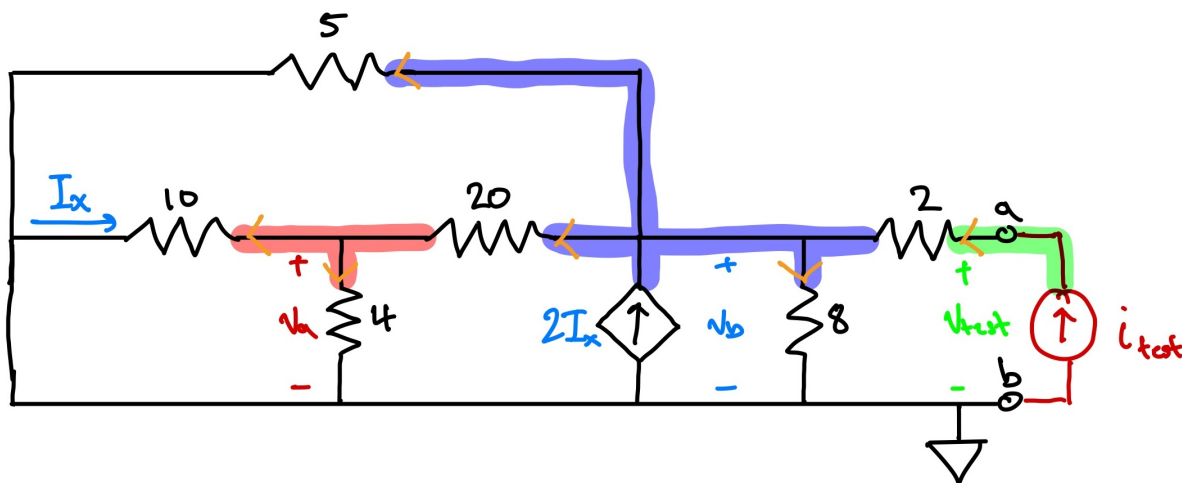Isolate the current source by setting the voltage source to 0,



KCLs,

$$\begin{aligned}
 \sum i &= \frac{v_b - v_a}{20} - \frac{v_a - 0}{4} - \frac{v_a - 0}{10} = 0 \\
 \sum i &= \frac{v_{test} - v_b}{2} + 2I_x - \frac{v_b - v_a}{20} - \frac{v_b - 0}{8} - \frac{v_b - 0}{5} = 0 \\
 \sum i &= i_{test} - \frac{v_{test} - v_b}{2} = 0
 \end{aligned}$$

i-v's,

$$I_x = -\frac{v_a - 0}{10}$$

Solve for v''_{test} ,

$$\begin{aligned}
 \frac{v_b - v_a}{20} - \frac{v_a - 0}{4} - \frac{v_a - 0}{10} &= 0 \\
 v_b - v_a - 5v_a - 2v_a &= 0 \\
 v_b - 8v_a &= 0
 \end{aligned}$$

$$v_b = 8v_a$$

$$\begin{aligned} \frac{v_{test} - v_b}{2} + 2I_x - \frac{v_b - v_a}{20} - \frac{v_b - 0}{8} - \frac{v_b - 0}{5} &= 0 \\ 10v_{test} - 10v_b + 40I_x - v_b + v_a - \frac{5}{2}v_b - 4v_b &= 0 \\ 10v_{test} - 10v_b - 4v_a - v_b + v_a - \frac{5}{2}v_b - 4v_b &= 0 \\ 10v_{test} - 80v_a - 4v_a - 8v_a + v_a - 20v_a - 32v_a &= 0 \\ 10v_{test} - 143v_a &= 0 \\ 10v_{test} &= 143v_a \\ v_a &= \frac{10}{143}v_{test} \end{aligned}$$

$$\begin{aligned} i_{test} - \frac{v_{test} - v_b}{2} &= 0 \\ 2i_{test} - v_{test} + v_b &= 0 \\ 2i_{test} - v_{test} + 8v_a &= 0 \\ 2i_{test} - v_{test} + \frac{80}{143}v_{test} &= 0 \\ 2i_{test} - \frac{63}{143}v_{test} &= 0 \\ v_{test}'' &= \frac{286}{63}i_{test} \end{aligned}$$

Plug back into v_{test} ,

$$\begin{aligned} v_{test} &= v_{test}' + v_{test}'' \\ v_{test} &= \frac{1102}{63} + \frac{286}{63}i_{test} \end{aligned}$$

Thevenin equivalent,

$$\begin{aligned} v_{test} &= v_{th} + R_{th}i_{test} \\ v_{test} &= \frac{1102}{63} + \frac{286}{63}i_{test} \\ v_{test} &= \boxed{17.492 \text{ V} + 4.540 \Omega i_{test}} \end{aligned}$$