
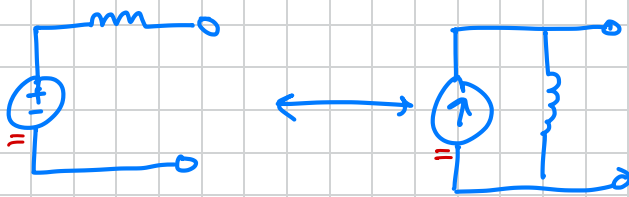
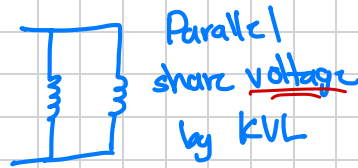


DUALITY

KVL $\sum \underline{v} = 0$

KCL $\sum \underline{i} = 0$

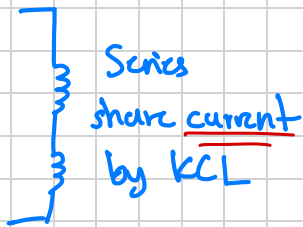
★ exchanging the roles of voltage and current



Duality: If two components share current by virtue of KCL \Rightarrow series.

If two components share voltage by virtue of KVL \Rightarrow parallel

Voltage	\longleftrightarrow	Current
Across	\longleftrightarrow	Through
Short	\longleftrightarrow	Open
Parallel	\longleftrightarrow	Series
KVL \rightarrow loops	\longleftrightarrow	KCL \rightarrow nodes
Outer loop	\longleftrightarrow	Ground Node
Resistor	\longleftrightarrow	Conductance

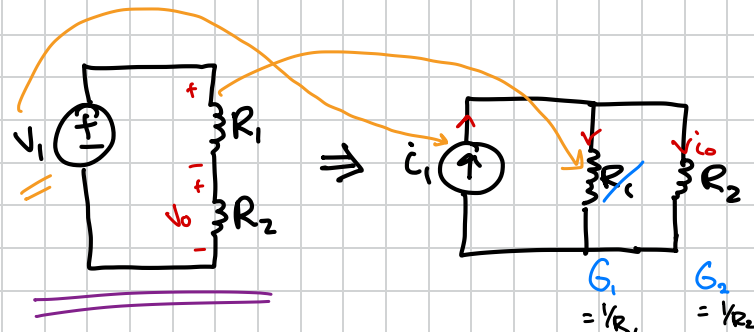

A voltage divider has a voltage source in series with two resistors. The output is the voltage across the 2nd resistor.
A current divider has a current source in parallel with two resistors. The output is the current through the 2nd resistor.

$$V_0 = \frac{R_2}{R_1 + R_2} V_1$$


$$i_0 = \frac{V}{R_2} = \left(\frac{R_1}{R_1 + R_2} i_1 \right) \frac{1}{R_2} = \frac{R_1}{R_1 + R_2} i_1$$

some error


A resistor is a linear voltage-current relationship when $v = i \times \text{const}$ [const] = $\frac{\text{Volts}}{\text{amps}}$ (ohms Ω)

A conductance is a linear current-voltage relationship when $i = v \times \text{const}$ [const] = $\frac{\text{amps}}{\text{Volts}}$ (siemens S)
conductance

In one circuit, $R = \frac{1}{G}$

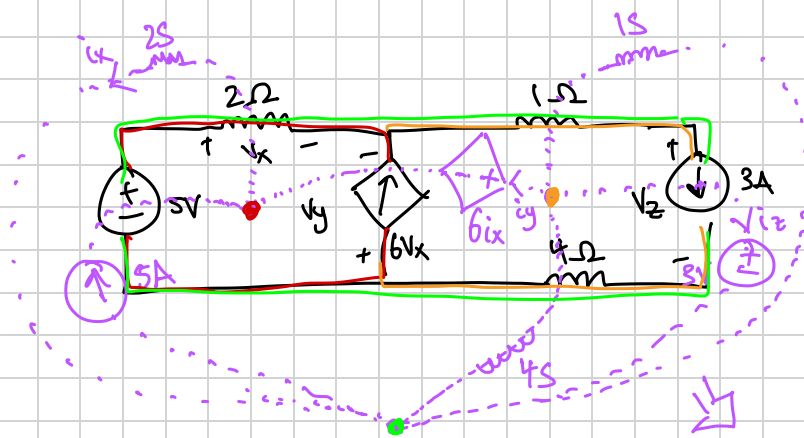

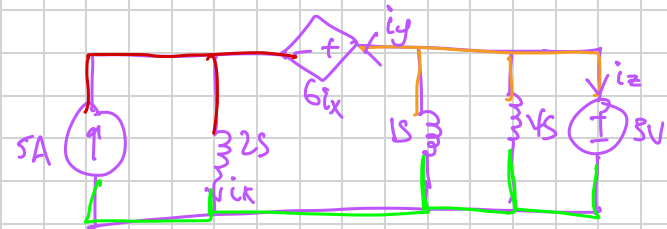Draw node for each mesh
Draw node outside for outer loop



Label voltage across each component

If v counts as $(+)$ when KVL clockwise,
then the dual i is into dual node

If PSE in original, PSE apply