
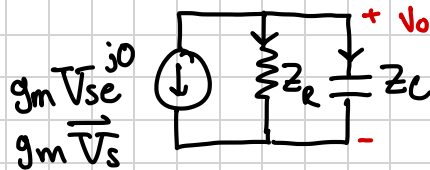


AC MOSFET

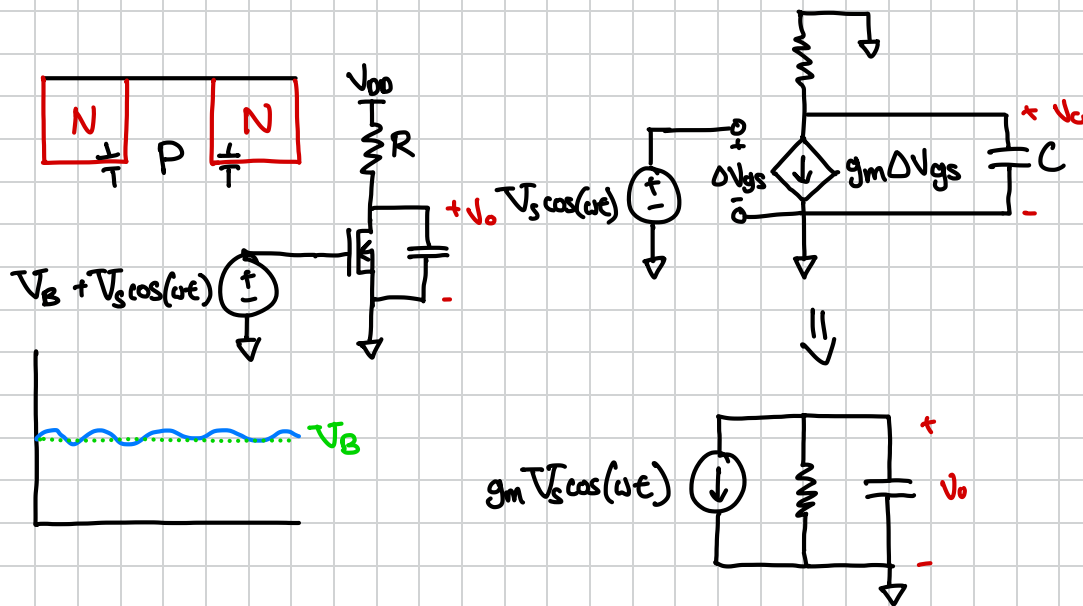

$$g_m \vec{V}_S + \frac{\vec{V}_o}{R} + \frac{\vec{V}_o}{Z_C} = 0$$

$$g_m \vec{V}_S + \frac{\vec{V}_o}{R} + \vec{V}_o \times j\omega C = 0$$

$$R g_m \vec{V}_S + \vec{V}_o + \vec{V}_o \times j\omega C = 0$$

$$TF = \frac{\vec{V}_o}{\vec{V}_S} = \frac{-g_m R}{1 + j\omega C R}$$

$$|TF| = \frac{g_m R}{\sqrt{1 + (\omega R C)^2}} = \frac{V_o}{V_S}$$

$$\angle TF = \tan^{-1}\left(\frac{0}{-1}\right) - \tan^{-1}\left(\frac{\omega R C}{1}\right)$$


$$= 180^\circ - \tan^{-1}\left(\frac{\omega R C}{1}\right)$$

$$TF = |TF| e^{j\angle TF}$$

PLOT $|TF|$ dB VS ω log

$$|TF|_{\text{low freq}} \approx g_m R = g_m R \times \omega^0 \text{ Slope} = 0 \frac{\text{dec}}{\text{dec}} = 0 \frac{\text{dB}}{\text{dec}}$$

$$|TF|_{\text{high freq}} \approx \frac{g_m R}{\omega R C} = \frac{g_m}{\omega C} = \frac{g_m}{C} \times \omega^{-1} \text{ Slope} = -1 \frac{\text{dec}}{\text{dec}} = -20 \frac{\text{dB}}{\text{dec}}$$

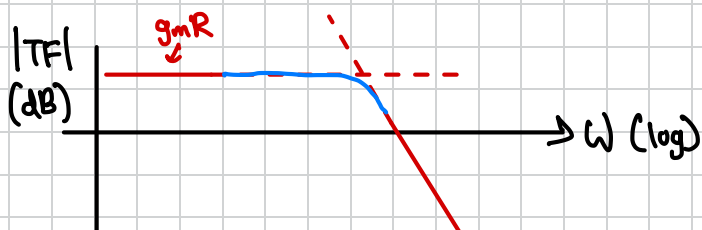

$$\omega = \frac{1}{RC} \quad |TF| = \frac{g_m R}{\sqrt{2}}$$

$$\Delta V_o = |TF| V_i \cos(\omega t + \angle \vec{V}_i + \angle TF)$$