



Basic Gates

↑
Inside are
transistors


Functions of a transistor

① Amplification (Boost Signal)

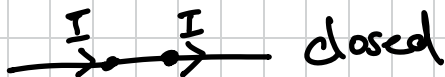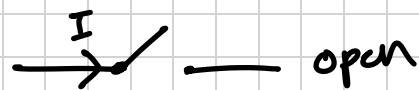
② Switch ★ Circuits → VLSI Very Large Scale Integration




Transistor (n-type)

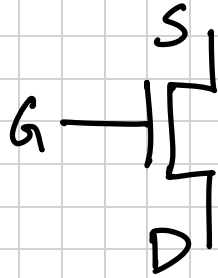

G	Switch state
0	open
1	closed

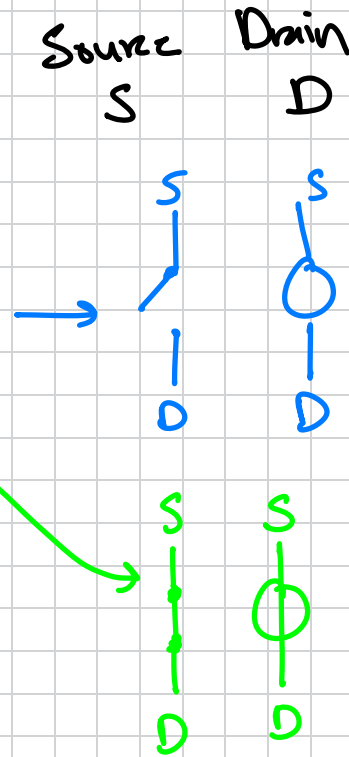

Transistor (p-type)

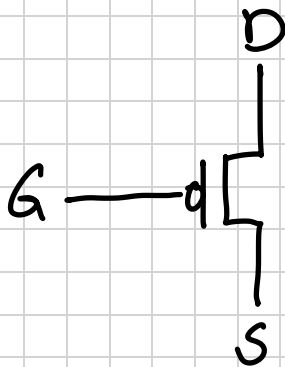

G	Switch state
0	closed
1	open


metal + semiconductor
NMOS

metal + resistor
FET



MOSFET

NMOS + PMOS = CMOS


NOT gate

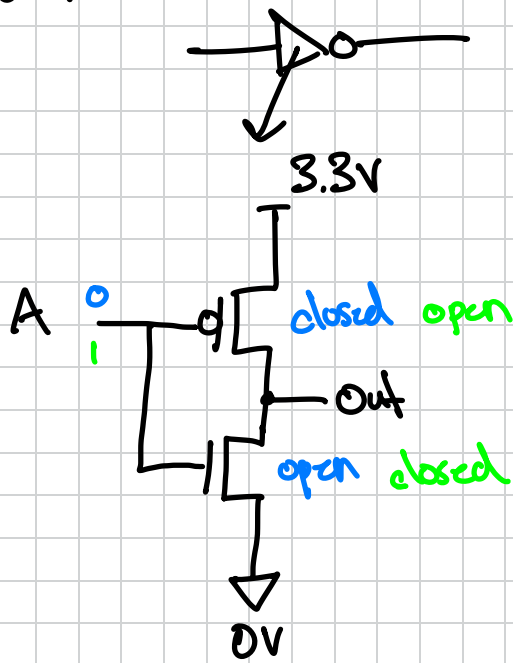



A	out
0	1
1	0

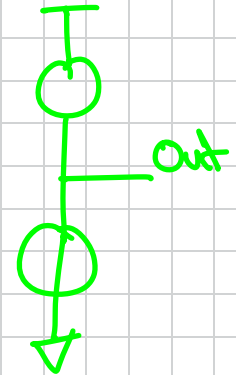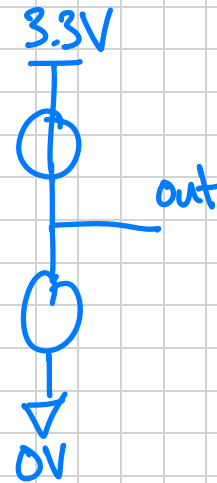


What if?

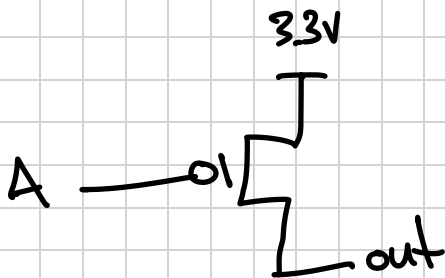


A	out
0	1
1	floats

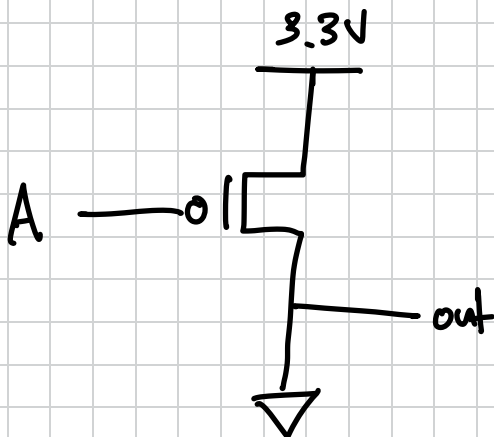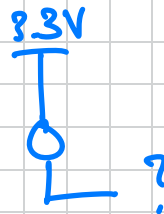

A	out
0	HiZ

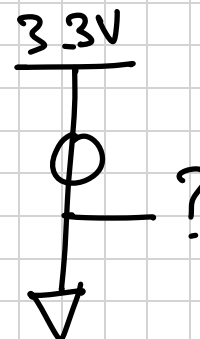


NAND

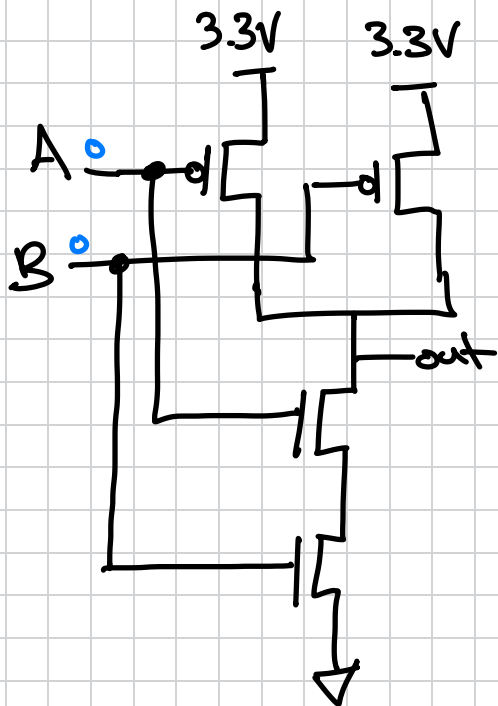

$$A \quad B \quad \text{---} \text{---} \text{---} \text{---} \text{---} (AB)'$$

A	B	A NAND B
0	0	1
0	1	1
1	0	1
1	1	0

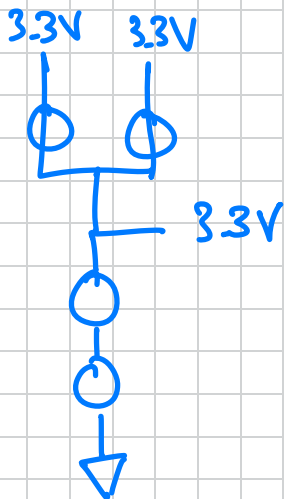

A	B	XOR
0	0	0
0	1	1
1	0	1
1	1	0

$$\bar{A}B + A\bar{B}$$